

20/11/19

1. Measuring Instruments

Measurement:- The result obtained by comparing unknown quantity with known quantity is called Measurement.

Measuring Instruments:- The instruments used for measurements are called measuring instruments.

→ The electrical quantities like power, current, voltage, resistance are to be measured with the help of measuring instruments.

Necessary Requirements:-


→ With the introduction of the instrument, the circuit parameters shouldn't be altered in the circuit.

→ The instrument must and should consume less amount of power.

Classification of Measuring Instruments:-

The measuring instruments are classified as follows

classification

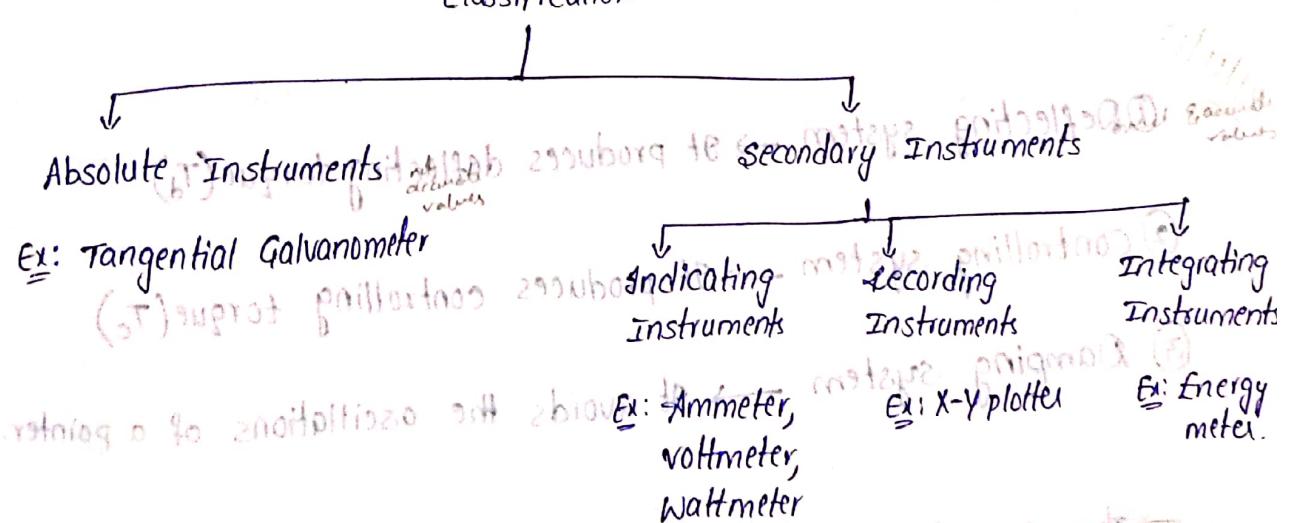

Absolute Instruments:- These instruments are used in laboratories. The unknown quantity is measured in terms of instrument parameter.
Ex: Tangential Galvanometer.

Secondary Instruments

the instruments which are used for indicating the magnitude of measured quantity.

① Indicating Instruments :- It consists of a standard dial & pointer. The pointer moves on standard dial the unknown quantity is calculated.
Ex: Ammeter, voltmeter & wattmeter

② Recording Instruments :- The unknown quantity is measured & recorded in the graph w.r.t time.
Ex: X-Y plotter

③ Integrating Instruments :- The unknown electricity is measured over a period of time.
Ex: Energy meter, watt-hour meter

Essential requirements of any Indicating Instruments :-

① Deflecting system

② controlling : $\tau_c \rightarrow$ opposite direction to deflecting torque

③ Damping :- to avoid oscillations

21/11/19
① Deflecting system \rightarrow It produces deflecting torque (T_d)

② Controlling system \rightarrow It produces controlling torque (τ_c)

③ Damping system \rightarrow It avoids the oscillations of a pointer.

\rightarrow The deflecting torque acting on the pointer to move in forward direction from its zero position. The deflecting torque can be produced in any of the following methods.

(i) Magnetic effect

(ii) Electrostatic effect

(iii) Induction effect

(iv) Thermal effect.

(i) Magnetic effect:-

Whenever a current carrying conductor is placed in uniform magnetic field there exists a force on the conductor. This effect is used in Ammeters, Voltmeters, Wattmeters.

(ii) Electrostatic effect:-

When two charged plates are brought nearer there exists a force. This type of effect is used in electrostatic voltmeters.

(iii) Induction effect:-

When AC supply is given to the magnets alternating current flows which cuts the disc. An emf is induced in it. Disc is closed path, current flows through it, interaction of disc flux & magnetic flux, the disc rotates. It is used in induction type Energy meters.

(iv) Dissimilar Thermal effect:-

When two dissimilar materials joined together to form a closed loop, these metals are maintained with different temperatures, an emf is induced in it and the current will be flow. This current is used to produce a torque.

2) Controlling system:-

The controlling system provides controlling torque which serves two functions,

- ① When the supply is removed, pointer bring backs to original zero position.
- ② It provides equal and opposite torque to make pointer at definite value.


There are 2 methods for controlling system

- ① Spring control method

- ② Gravity control method.

- ① Spring Control method :-

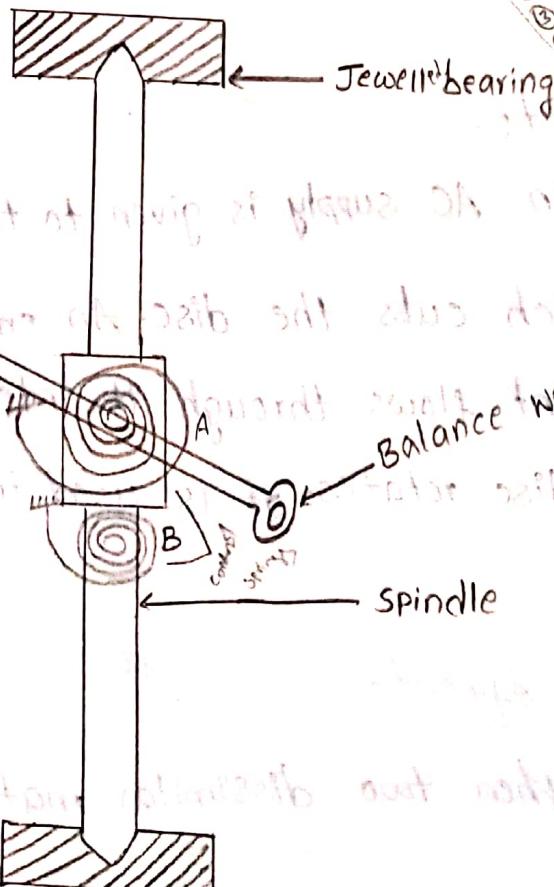Spring should have following qualities:
① low resistance
② It should be non-magnetic
③ consist of small resistors sufficient current
④ free from mechanical stress



The controlling torque

$$T_c = \frac{E b t^3}{12 L} * \theta \quad \text{N-m}$$

→ where, E = young's modulus of a material N/m^2

b = Depth of spring

t = thickness of spring

L = Length of spring

D = Deflection

$$T_c = K_s \theta$$

→ the deflecting torque,

$$T_d = K \cdot I$$

At equilibrium condition,

$$T_d = T_c$$

$$K_s \theta = K I$$



$$\therefore I \propto \theta$$

22/11/19

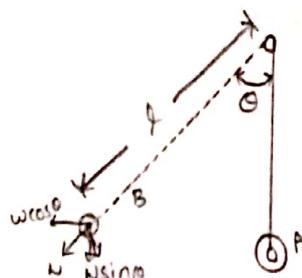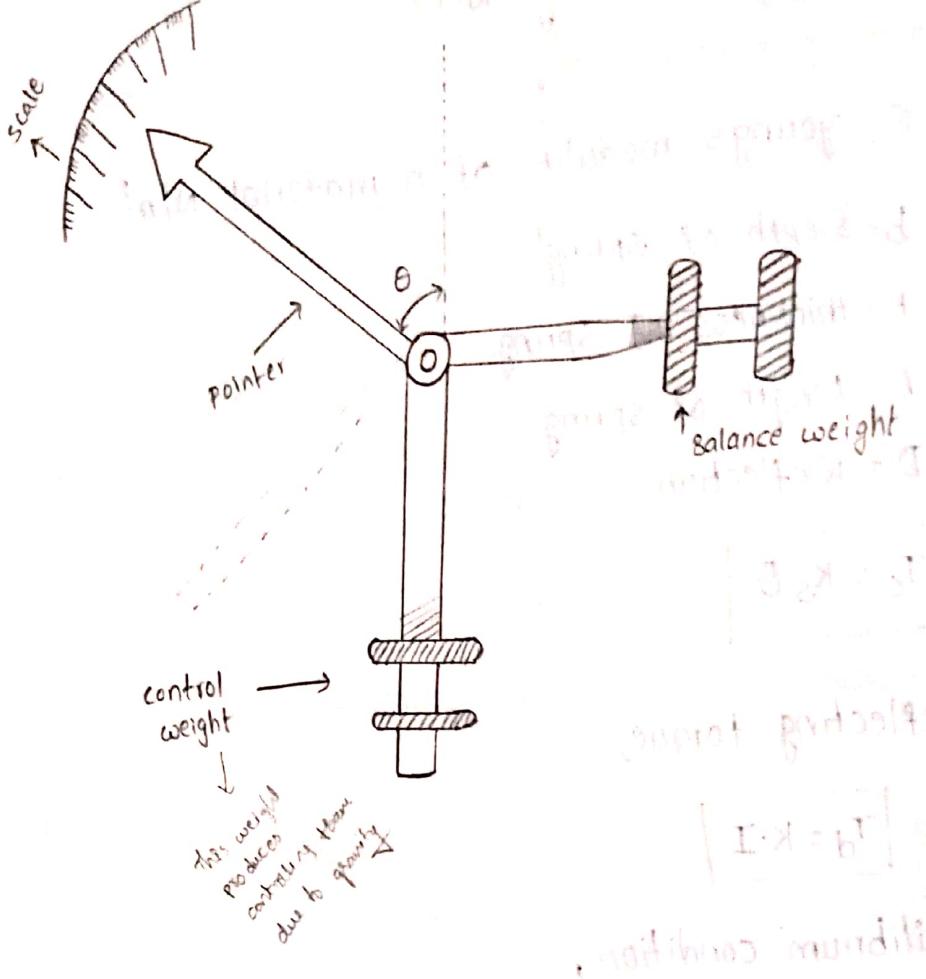(a) Gravity control method:-

It is used for vertically mounted instruments.

the control weight is also adjustable but the scale is non-uniform



→ The controlling torque

$$T_c = w \sin \theta * l$$

where $K = w * l$

∴ controlling torque $T_c = K \sin \theta$

Reflecting torque $T_d = K I$

At equilibrium condition

$$T_d = T_c$$

$$I \propto \sin \theta$$

Scale is non-uniform.

$$\alpha T = \beta T$$

$$T \propto \sin \theta$$

$$\theta \propto T^{\frac{1}{2}}$$

Advantages of gravity control

① Time independent

② Temperature independent

③ controlling torque is nearly varying control weight

④ Simple & cheap

Disadvantages

① Scale non-uniform

② used only for vertically mounted instruments

③ Requires proper leveling, otherwise causes serious errors.

Differences between Spring control & gravity control.

Spring control	Gravity control.
$I = \frac{EJ}{l^3}$	with help of springs the pointer backs to original position even if it is not there due to being back to zero position
disprings are using	Teaching notes
1. scale is uniform i.e., $I \propto \theta$	1. scale is non-uniform i.e., $I \propto \sin\theta$
2. gt is used in all instruments	2. gt is only used in vertically mounted instruments.
3. control weight is fixed	3. control weight is adjustable by adjusting wt of system
4. this method gives accurate values.	4. the readings taken are not an accurate values.
5. this method involves more cost.	5. cost is less
6. Leveling is not required	6. proper levelling is required to get accurate values.

Damping system:-

There are 3 types of Damping systems

- ① under damped system
- ② over damped system
- ③ critically damped system.


Under Damping system:- In this system, the pointer will take some time to settle at final position.

Over Damped system:- In this system, the pointer is sluggish & lazy.

takes more time to settle at final steady position.

Critically Damped system:- In this system, the pointer placed at final steady position rapidly & quickly.

23/11/19

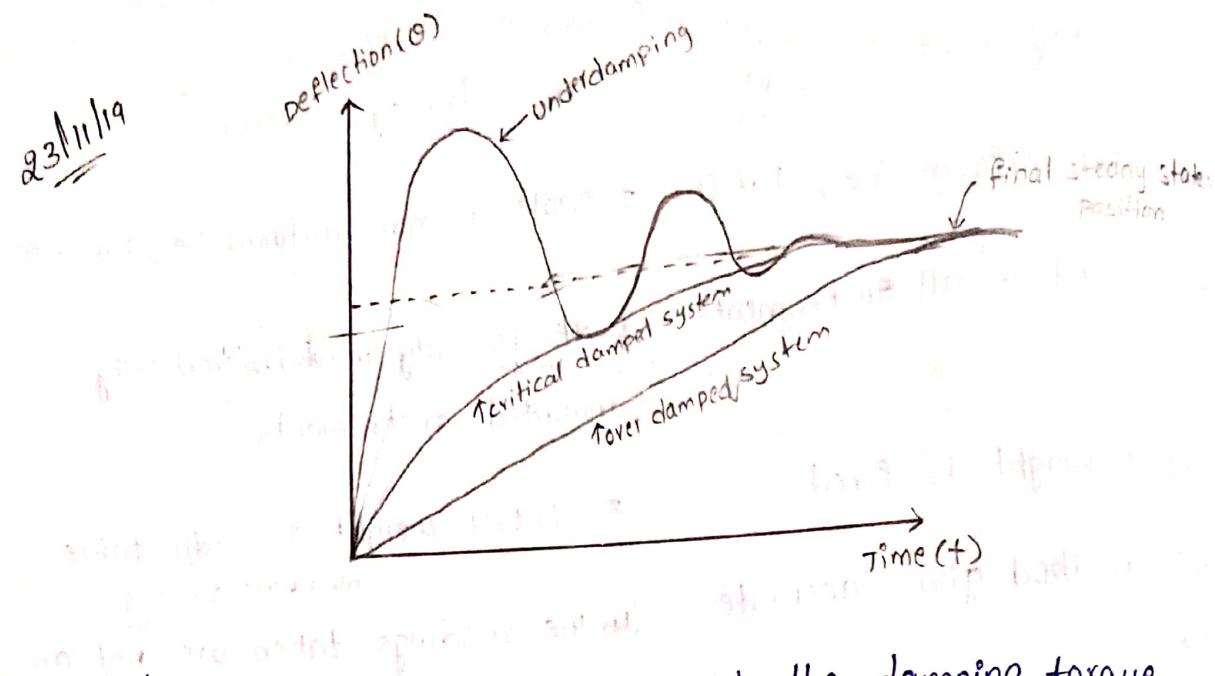


* There are three methods to provide the damping torque

1. Air friction Damping



2. oil / fluid friction Damping

3. Eddy current Damping
↓ it is best

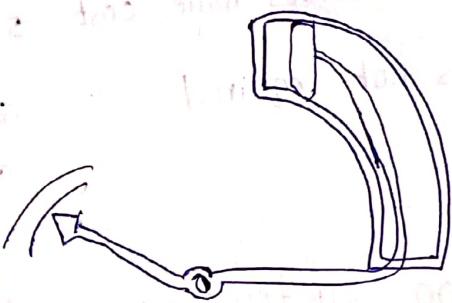

1. Air friction Damping :-

→ working principle to damp is no small

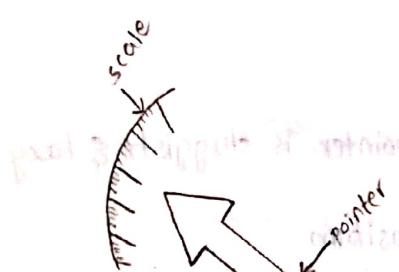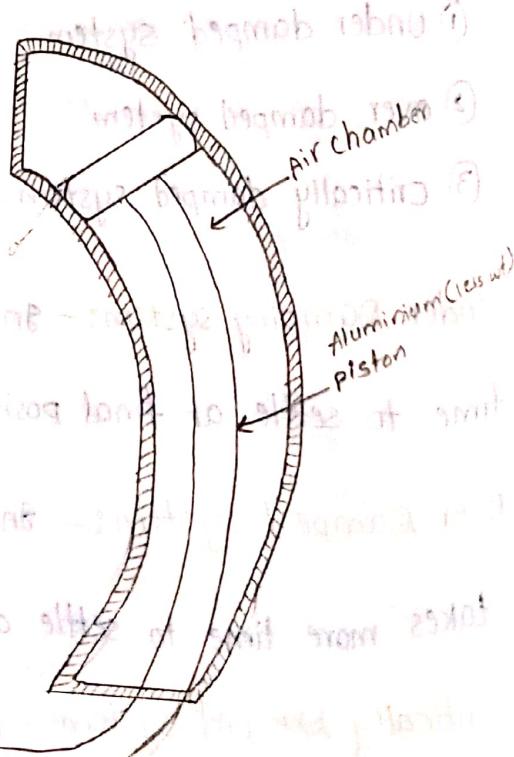



4. To break rotating

→ It consists of a light aluminium piston in the air chamber. The clearance between Air chamber and piston is very less.

→ when the piston moves outside the chamber (from motion) outside air opposes a piston direction.

→ When the piston moves into the chamber, air inside is compressed. Therefore, for to and fro motions piston reciprocates in the air chamber. Hence, oscillations are avoided.

2. Fluid / oil Friction Damping:-

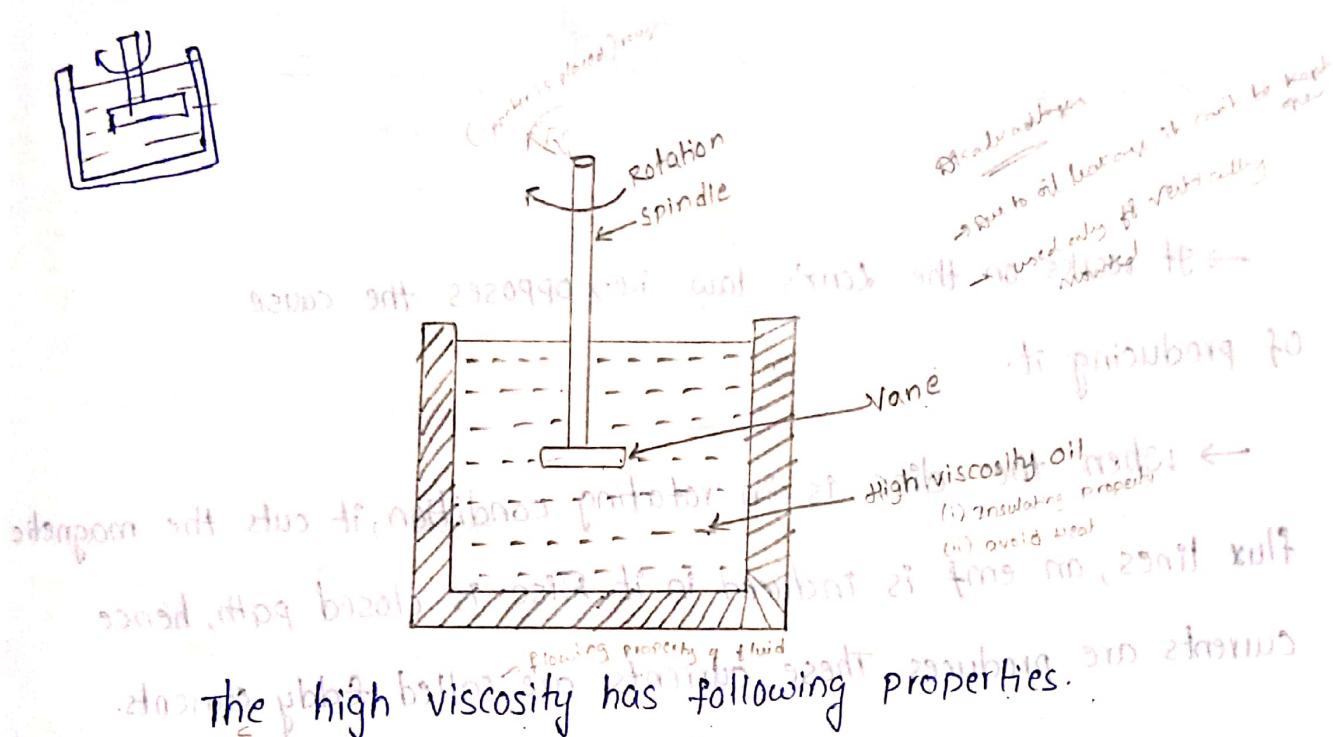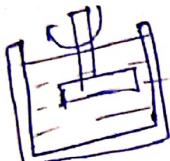


- Advantages

 - (i) It is acting as a insulating medium for inner parts.
 - (ii) It provides cooling.
 - (iii) Due to upthrust of a oil, the bearings are free from frictional losses.

→ when the vane is rotating the direction is opposed by high viscosity oil. Hence, the oscillations are avoided.

3. Eddy current Damping:-

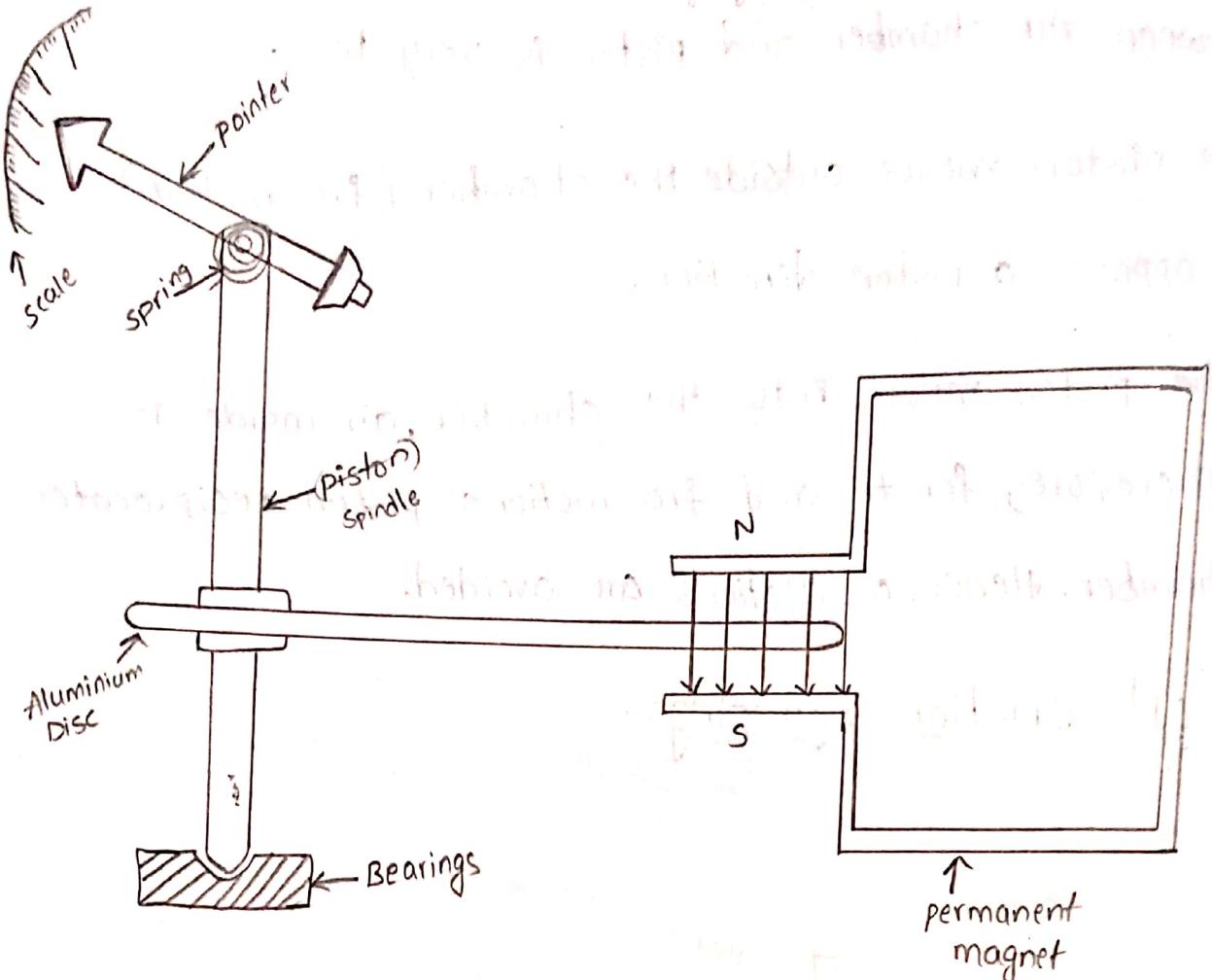

dynamically
induced emf
[conductivity
more, magnetic field
constant]
Lenz's law (opposite to
cause of producing)

→ It works on the Lenz's law i.e., opposes the cause of producing it.

→ When the disc is in rotating condition, it cuts the magnetic flux lines, an emf is induced in it. Disc is closed path, hence currents are produced. These currents are called eddy currents.

→ The eddy currents oppose the rotation of disc. Hence, oscillation are avoided.

→ It is the most efficient & effective method of Damping system.

25/11/19

→ It is unipolar device.


8M

Permanent Magnet Moving coil:— [PMMC]


①

→ This instrument is used for measurement of DC quantities accurately. It is operated by a motoring principle. i.e., whenever a current carrying conductor is placed in uniform magnetic field, the conductor experiences a force (or) Torque.

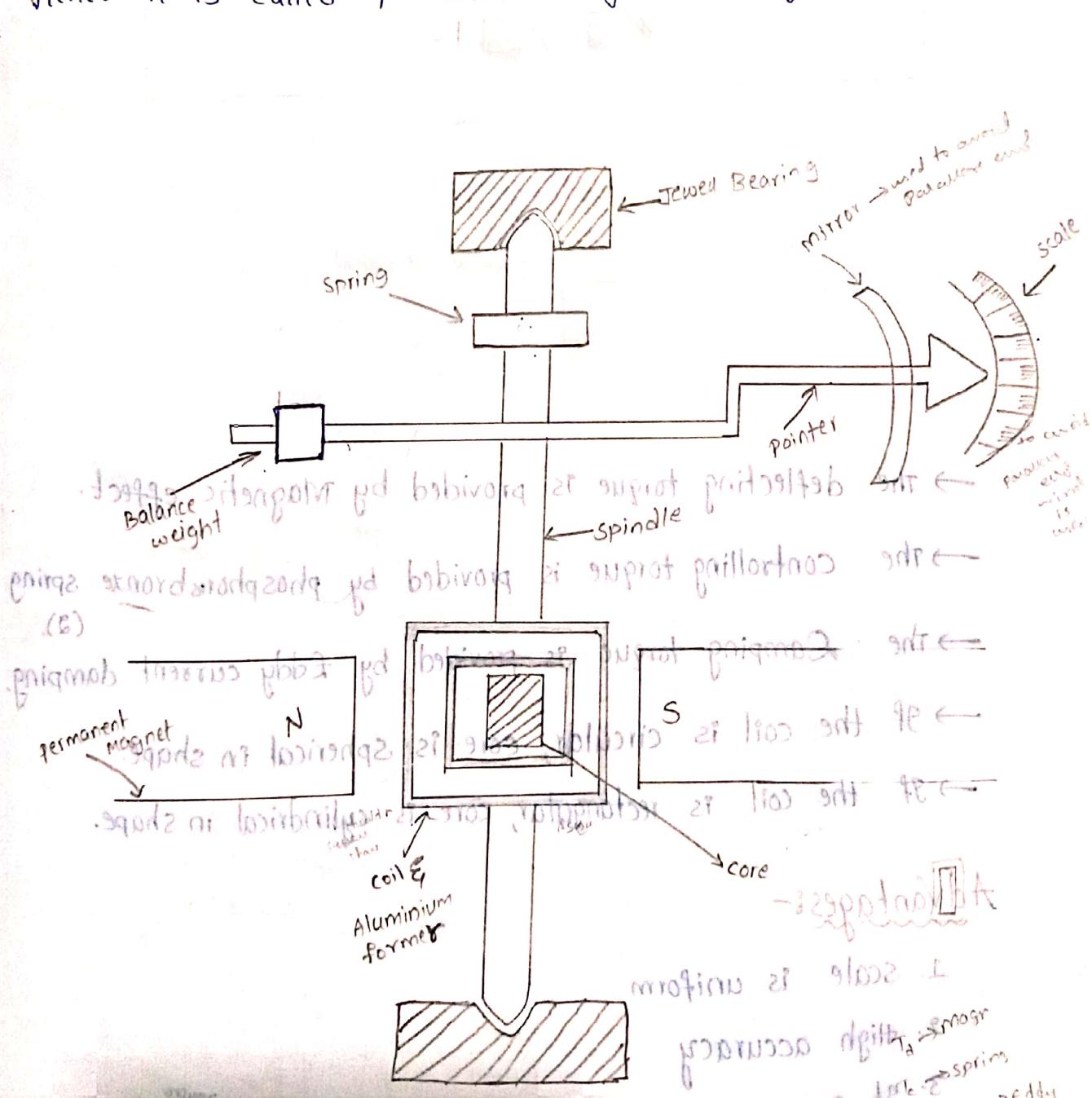→ The coil is moving and magnets are permanent. Hence it is called permanent magnet moving coil instrument.



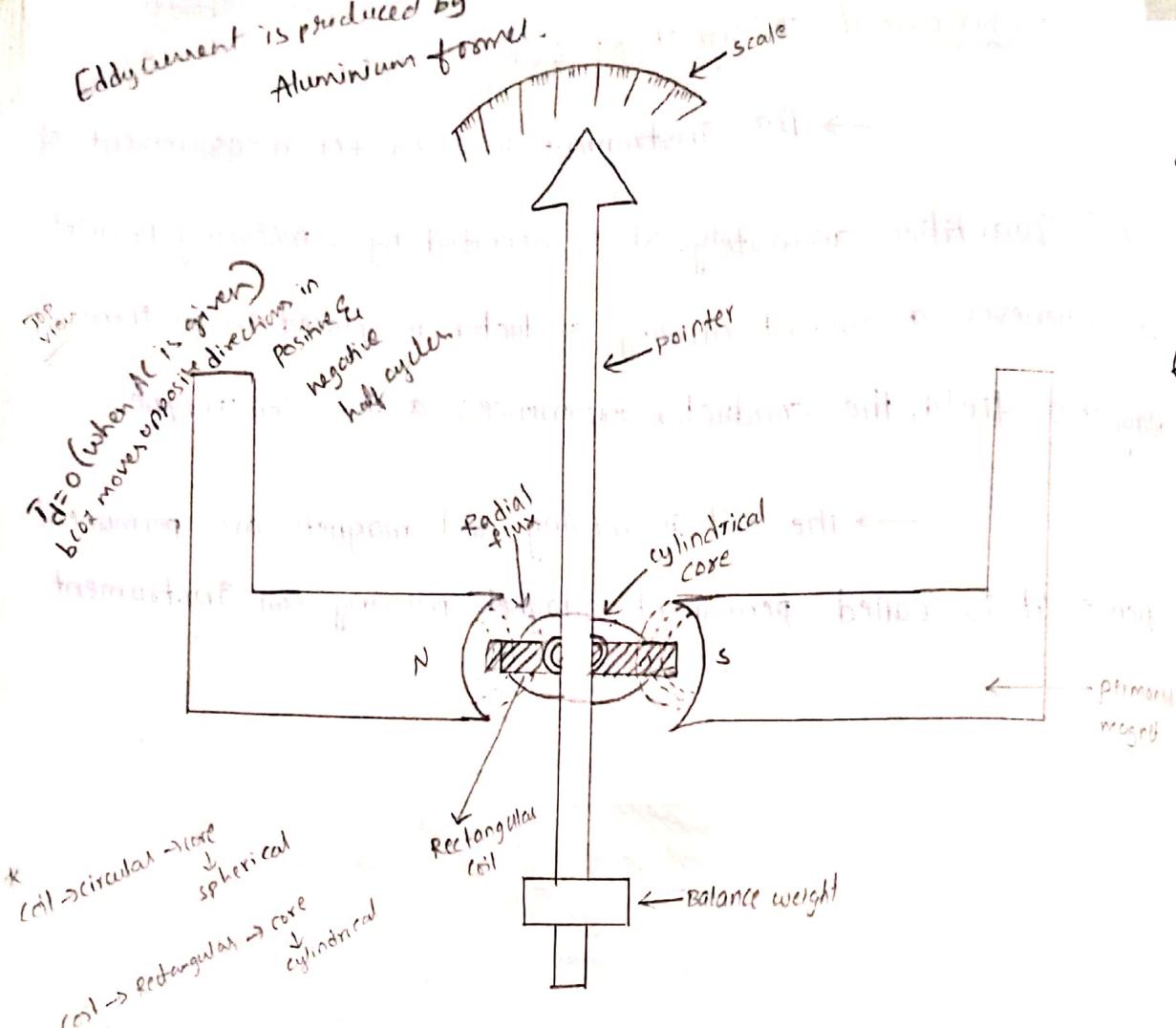Eddy current is produced by
Aluminum former.



→ the deflecting torque is provided by magnetic effect.

→ the controlling torque is provided by phosphor-bronze spring (2).

→ the Damping torque is provided by eddy current damping.

→ If the coil is circular, core is spherical in shape.

→ If the coil is rectangular, core is cylindrical in shape.

Advantages:-

for radial flux

1. scale is uniform

2. High accuracy

3. It consumes less power i.e., $25 \mu\text{W}$ to $200 \mu\text{W}$ micro

4. Torque to weight (T/w) ratio is ~~high~~, hence frictional errors are avoided.

Disadvantages:-

1. cost of instrument is high
2. Due to aging of springs, errors are produced
3. It is only suitable for measurement of DC quantities, not for AC.

Torque Equation:-

the deflecting torque

$$T_d = NBAI$$

where, T_d = Deflecting torque in N-m

N = Number of turns on a coil

B = Flux Density in wb/m^2 (δ) Tesla

A = Area of cross-section of coil in m^2 .

I = current through the coil in Amperes.

$$T_d = GI \quad \rightarrow ①$$

$G = NBA = \text{constant}$ [Displacement constant]

→ the controlling torque

$$T_c = K_s \theta$$

where, K_s = spring constant in Nm/rad (or) Nm/Degree

$$K_s = \frac{Eb^3}{12L}$$

$$T \left[\frac{\text{N}}{\text{m}} \right] - (\theta) \text{ rad} = \text{Nm}$$

→ At final steady position

$$T_d = T_c$$

$$\therefore G I = K_s \theta$$

$$\therefore \text{Deflection } (\theta) = \left[\frac{G}{K_s} \right] I$$

here, $K = K_s$

$$\therefore I \propto \theta \quad \rightarrow \text{scale is uniform.}$$

Q1 A PMMC has a coil of dimensions $10\text{mm} \times 8\text{mm}$. The flux density in the air gap is 0.15 wb/m^2 . If the coil is wound for 100 turns carrying 5mA. calculate the deflecting Torque. calculate the deflection, if the spring constant (K_s) is $0.2 \times 10^{-6} \text{ Nm/degree}$.

Sol: Given Data,

$$\text{Area (A)} = 10\text{mm} \times 8\text{mm}$$

$$= 80 \text{ mm}^2 \quad [I = A B]$$

$$= 80 \times 10^{-6} \text{ m}^2$$

$$\text{Flux density in the air gap (B)} = 0.15 \text{ wb/m}^2$$

$$\text{Number of turns (N)} = 100$$

$$\text{current (I)} = 5\text{mA}$$

$$= 5 \times 10^{-3} \text{ A}$$

$$\text{Spring constant (Ks)} = 0.2 \times 10^{-6} \text{ Nm/degree.}$$

formula:-

→ Deflecting Torque is given by $T_d = N B A I$

$$T_d = N B A I$$

$$= 100 \times 0.15 \times 80 \times 10^{-6} \times 5 \times 10^{-3}$$

$$T_d = 6 \times 10^{-6} \text{ N-m}$$

$$\rightarrow \text{Deflection (\theta)} = \left[\frac{G}{K_s} \right] I$$

$$= \left[\frac{N B A}{K_s} \right] I$$

$$= \left[\frac{100 \times 0.15 \times 80 \times 10^{-6}}{0.2 \times 10^{-6}} \right] \times 5 \times 10^{-3}$$

$$\theta = 30^\circ \Rightarrow 30 \text{ degrees}$$

② The following data refers to a moving coil voltmeter.

Resistance = 10,000 Ω ; Dimensions of a coil = 30 mm \times 30 mm;

No. of turns of coil = 100; Flux density in air gap = 0.08 wb/m²;

Spring constant (K_s) = 3×10^{-6} Nm/degree. Find the deflection produced for voltage of 200 volts.

Sol: Given Data,

$$R = 10,000 \Omega$$

$$A = 900 \times 10^{-6} \text{ m}^2$$

$$N = 100$$

$$B = 0.08 \text{ wb/m}^2$$

$$K_s = 3 \times 10^{-6} \text{ Nm/degree}$$

$$V = 200 \text{ V}$$

$$\therefore I = \frac{V}{R} = \frac{200}{10,000} = 0.02 \text{ A}$$

$$\rightarrow T_d = NBAI$$

$$= 100 \times 0.08 \times 900 \times 10^{-6} \times 0.02$$

$$T_d = 144 \times 10^{-6} \text{ N-m}$$

$$\rightarrow \text{Deflection } (\theta) = \left[\frac{G}{K_s} \right] I$$

$$= \frac{144 \times 10^{-6}}{3 \times 10^{-6}}$$

$$\theta = 48 \text{ degrees.}$$

$$\begin{aligned} T_d &= NBAI \\ T_c &= K_s \theta \\ NBAI &= K_s \theta \\ \theta &= \frac{NBAI}{K_s} \end{aligned}$$

③ The Deflecting torque (T_d) of an Ammeter varies as the square of the current passing through it. If a current of 5 Amps produces a deflection of 90 degrees, what will be the deflection for current of 10 Amps when the instrument (i) Spring controlled (ii) Gravity controlled.

Sol: Given data,

$$\begin{cases} \text{current } (I) = 5 \text{ Amps} \\ \text{deflection } (\theta) = 90^\circ \end{cases}$$

$$T_d = K_1 I^2 \quad \text{N-m}$$

(i) Spring control method:-

$$T_d = K_1 I^2 ; T_c = K_2 \theta$$

At equilibrium

$$T_d = T_c$$

$$K_1 I^2 = K_2 \theta$$

$$K_1 (5)^2 = K_2 (90^\circ)$$

$$\frac{K_1}{K_2} = 3.6 = K$$

$$\rightarrow T_d = K_1 I^2 ; T_c = K_2 \theta$$

$$= 3.6 \times (10)^2$$

$$T_d = 360 \text{ N-m}$$

At equilibrium

$$K_1 I^2 = K_2 \theta$$

$$K_1 (10)^2 = K_2 (\theta)$$

$$\theta = 3.6 \times 100$$

$$\theta = 360^\circ$$

(ii) Gravity control method:-

$$T_d = K I^2 ; T_c = \omega s \sin\theta \times l$$

$$T_c = K g \sin\theta$$

At equilibrium,

$$K I^2 = K g \sin\theta$$

$$\frac{K}{Kg} I^2 = \sin\theta$$

$$\sin\theta = 3.6 \times (10)^2$$

$$= \text{Math error}$$

In this control, if 10Amp of current is applied, the measurement is not possible.

26/11/19

Errors in PMMC Instrument:-

The following are the sources of errors

1. Frictional errors
2. Temperature errors
3. Aging of magnet & control springs.

→ The frictional errors are caused due to improper bearings. To avoid the frictional errors, T/w ratio must be high.

⇒ When the instrument is under operating condition, it causes/produces heat to avoid temperature errors. Large series resistance with low temperature co-efficient is used for voltmeters. 1shunt resistance for Ammeters.

⇒ Aging of permanent magnet and control springs causes the errors. If magnet is weak, it produces less ^{flux} deflection.

If the control spring is weaken, it produce large deflection. To reduce these errors, proper material is used during manufacturing.


Moving Iron Instruments:

→ Based on the working principle, these are classified as two types.

③ (i) Moving Iron attraction type.

④ (ii) Moving Iron repulsion type.

(i)

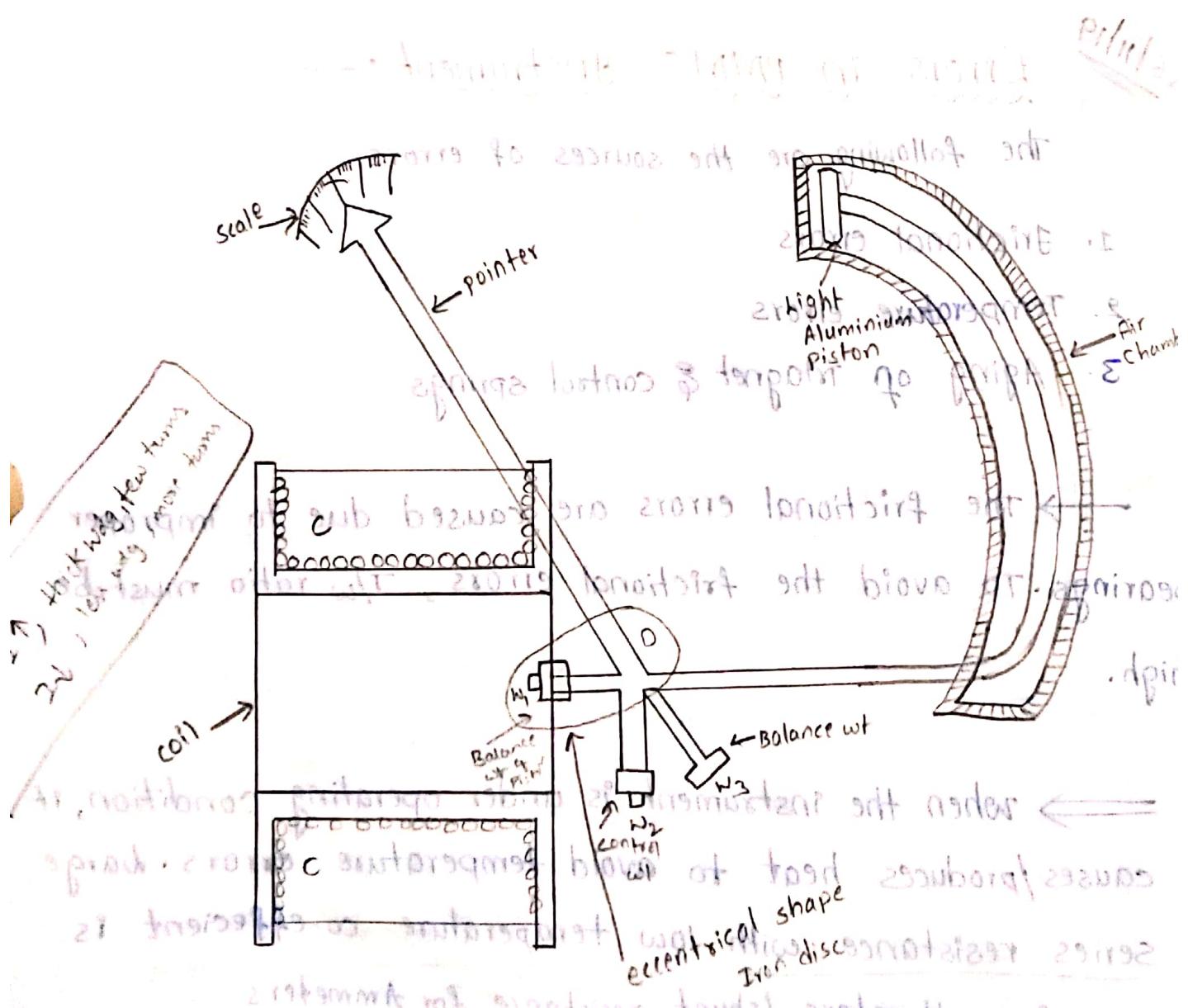

→ It works based on force of attraction principle i.e., whenever a iron piece is brought nearer to the magnet, it attracts.

→ The deflecting torque is produced by force of attraction.

→ The controlling torque is produced by either spring control

(or) Gravity control method.

→ The Damping torque is provided by Air friction Damping

→ It is used for AC quantities.

27/11/19

④ Torque equation of MI Instruments

Consider small increment current supplied to a coil of the instrument. Due to this current, the deflection is " $d\theta$ " and the deflecting torque is " T_d ". Hence, the mechanical work done

$$\therefore \text{Mechanical work done} = T_d \cdot d\theta \quad \rightarrow ①$$

Let "I" is initial current, " θ " is deflection, "L" is inductance.

EE = stored energy + Mechanical work

Inductance $L = \frac{dI}{dt}$ = change in current \Rightarrow $I = I_0 e^{bt}$ \Rightarrow $b^2 L = b^2 I_0 + b^2 I$

$$d\theta = \text{change in deflection}$$

$$b^2 L + b^2 I_0 + b^2 I = b^2 I_0 + b^2 I$$

$$dL = \text{change in inductance.}$$

Due to the change of voltage, the current increases.

$$\rightarrow e = \frac{d}{dt} [LI] \Rightarrow \text{voltage across coil} = \frac{1}{b} \frac{d}{dt} [b^2 I_0 + b^2 I] = b^2 I_0 + b^2 I$$

$$e = L \frac{dI}{dt} + I \frac{dL}{dt} \quad \rightarrow ②$$

→ Electrical Energy input

$$e^{idt} = \left[L \frac{dI}{dt} + I \frac{dL}{dt} \right] Idt$$

$$\text{RF Input} = LI dI dt + I^2 dL \xrightarrow{\text{③}} \text{input power}$$

→ The energy stored in a coil is $\frac{1}{2}LI^2$ increases to

$$\frac{1}{2}(L+dL)(I+dI)^2$$

→ change in stored energy

$$\Rightarrow \frac{1}{2}[L+dL][I+dI]^2 - \frac{1}{2}LI^2$$

$$= \frac{1}{2}[L+dL][I^2 + 2IdI + dI^2] - \frac{1}{2}LI^2$$

$$= \frac{1}{2}LdI^2 + LdIdI + \frac{1}{2}dI^2 + \frac{1}{2}I^2dL + IdI^2 + \frac{1}{2}dLdI$$

$$\text{snob} = \frac{1}{2}LdI^2 + LdIdI + \frac{1}{2}dI^2 + \frac{1}{2}I^2dL + IdI^2 + \frac{1}{2}dLdI$$

$$\text{④} \xrightarrow{\text{neglecting higher order terms}} \text{snob} = \text{snob}$$

→ Neglecting higher order terms

$$= LI dI + \frac{1}{2}I^2 dL \xrightarrow{\text{④}}$$

∴ Electrical Energy input = change in stored energy + Mechanical work done

$$LI dI + I^2 dL = LI dI + \frac{1}{2}I^2 dL + T_d \cdot d\theta$$

$$\therefore \frac{1}{2}I^2 dL = T_d \cdot d\theta$$

$$\therefore T_d = \frac{1}{2} \frac{I^2 dL}{d\theta}$$

$$\xrightarrow{\text{⑤}} \frac{b}{T_b} = 9 \leftarrow$$

→ controlling torque $T_c = K\theta \rightarrow ⑥$

→ At equilibrium condition, $T_d = T_c$

$$\frac{1}{2} I^2 \frac{dL}{d\theta} = K\theta$$

$$\therefore \text{Deflection } (\theta) = \frac{1}{2} \frac{I^2}{K} \frac{dL}{d\theta}$$

Q: The Inductance of a moving iron instrument is given by $L = (12 + 6\theta - \theta^2) \mu H$, where "θ" is deflection in radians.

From zero position, the spring constant is $12 \times 10^6 \text{ nm/radians}$.

Calculate the deflection for a current of 8 Amps.

Sol: Given Data,

$$L = [12 + 6\theta - \theta^2] \mu H$$

$$K = 12 \times 10^6 \text{ nm/radians}$$

$$\therefore \text{Deflection } (\theta) = \frac{1}{2} \frac{I^2}{K} \frac{dL}{d\theta}$$

$$= \frac{1}{2} \times \frac{(8)^2}{12 \times 10^6} \times \frac{d(12 + 6\theta - \theta^2) \mu}{d\theta}$$

$$= \frac{1}{2} \times \frac{64}{12 \times 10^6} \times (6 - 2\theta) \mu$$

$$= 2.666 [6 - 2\theta]$$

$$\theta = 16 - 5.332 \theta$$

$$\theta = \frac{16}{6.332}$$

$$\therefore \theta = 2.526 \text{ radians}$$

$$1 \text{ radian} = \frac{180}{\pi} \text{ degrees}$$

$$2.526 \times \frac{180}{\pi} = 144.72 \text{ degrees}$$

2. The Inductance of a moving iron instrument is given by
 $L = [10 + 5\theta - \theta^2] \mu H$, where "θ" is the deflection in radians
 From zero position, the spring constant is $12 \times 10^{-6} \text{ Nm/radians}$.
 Estimate the deflection for a current of 5Amps.

Sol: Given Data,

$$L = [10 + 5\theta - \theta^2] \mu H$$

$$K = 12 \times 10^{-6} \text{ Nm/rad}$$

$$I = 5 \text{ A}$$

$$\theta = \frac{1}{2} \frac{I^2}{K} \frac{dL}{d\theta}$$

$$\therefore \theta = \frac{1}{2} \frac{I^2}{K} \frac{dL}{d\theta}$$

$$\theta = \frac{1}{2} \times \frac{(5)^2}{12 \times 10^{-6}} \cdot [5 - 2\theta]$$

$$\theta = 1.0416 [5 - 2\theta]$$

$$\theta + 2.0832\theta = 5.208$$

$$\therefore \theta = 1.689 \text{ radians}$$

In degrees ($\frac{\pi}{180}$) → not exact

~~$$4. (\theta - \theta = 0.029) \times \frac{180}{\pi(8) \times 1} =$$~~

~~$$4(0.029) \times \frac{180}{\pi(8) \times 1} =$$~~

(ii) Moving Iron Repulsion type Instruments :-

These are classified as two types.

(i) Radial Vane type

(ii) Co-axial vane type (8) Concentric vane type.

(i) Radial Vane type MI Instrument :-

→ It consists of two vanes [fixed & movable].

Fixed vane is attached to coil & movable vane is attached to spindle.


→ When the supply is given to the instrument on both the vanes same magnetic poles are created. Hence, the repulsive force is produced in between two vanes.

→ The movable vane rotates, attached spindle rotates and the pointer deflects on the scale.


→ Deflecting torque (T_d) is produced by repulsive force.

→ Controlling torque (T_c) is provided by spring control.

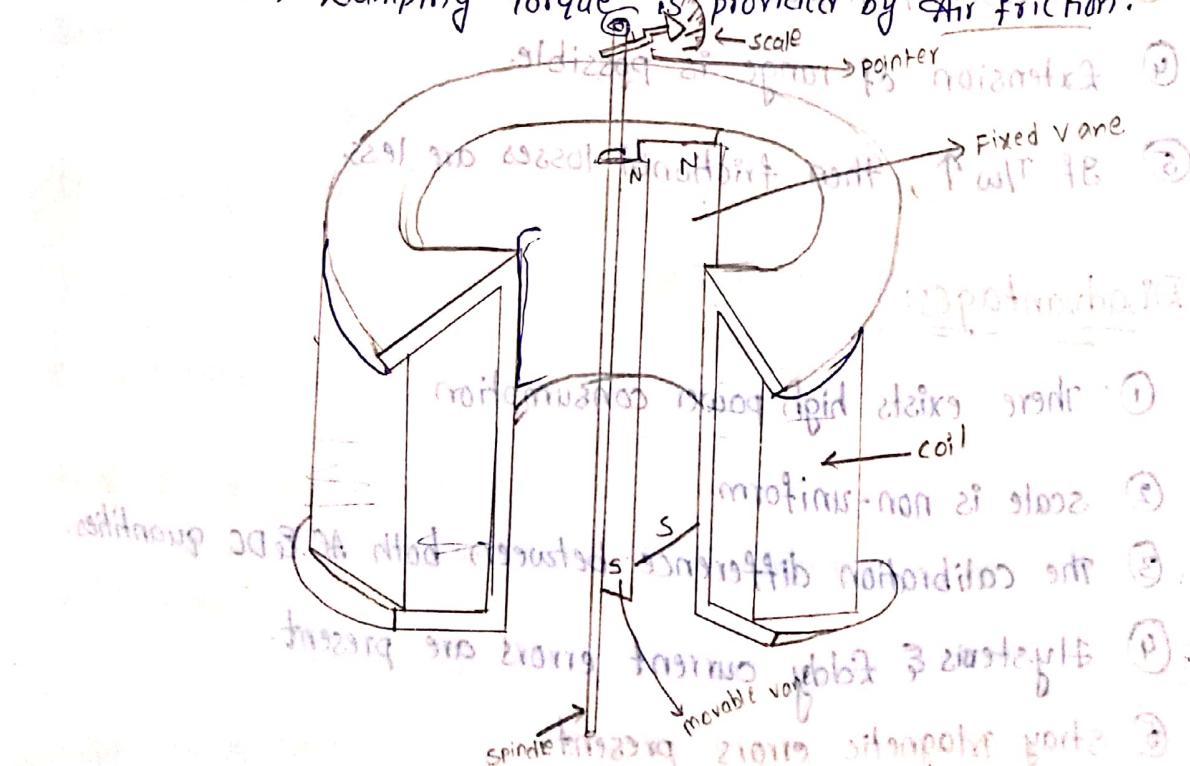
→ Damping torque is provided by Air friction.



(ii) Co-axial Vane type (d) concentric

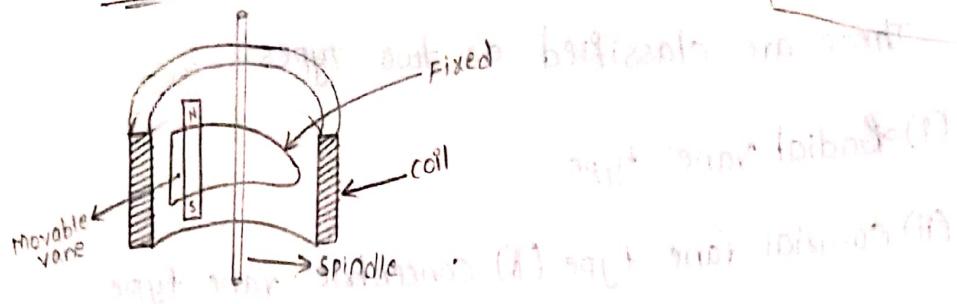

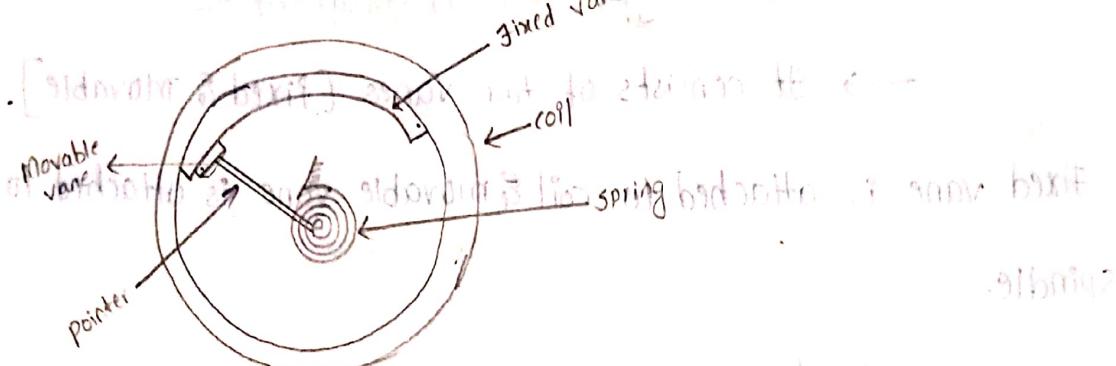T equation, "G" is same
as Attraction
for Repulsion



Force exerted left at inner vane of plates, left under S →
left point right. ^{radial} _{Some} operator as ^{Attraction} _{Repulsion} hence error left added to
equation out present in formula of error equation

Advantages:-

- ① It is used for measurement of both AC & DC quantities.
- ② Its construction is rigid & reliable.
- ③ The cost of instrument is less.
- ④ Extension of range is possible.
- ⑤ If $T/w \uparrow$, then frictional losses are less.

Disadvantages:-

- ① There exists high power consumption
- ② Scale is non-uniform
- ③ The calibration difference between both AC & DC quantities.
- ④ Hysteresis &ddy current errors are present.
- ⑤ Stray magnetic errors present.

28/11/19

Errors in Moving Iron Instruments:-

The following are the sources of errors:-

1. Temperature Error
2. Square stray Magnetic field Error
3. Hysteresis error
4. Eddy current Error
5. Frequency Error

1. When the instrument is under working condition, heat will be produced. This heat raises the temperature. To avoid these errors, coil is connected with resistance of low temperature coefficient.

Stray Magnetic field Error

2. Inside magnetic field due to primary coil, effect of outside flux effects the useful flux. So the deflecting torque reduces which causes errors. To avoid this, instrument is provided with shielding (or) casing.

Hysteresis error:-

When the instrument is supplied with AC supply it undergoes magnetization and Demagnetization. It is called Hysteresis effect. For quick Demagnetization small iron pieces are attached to coil.

Eddy current error:-

These depends on the frequency error.


Frequency Error:-

→ When the frequency changes, [$X_L = 2\pi f L$]; reactance

changes, current decreases, Deflecting torque (T_d) decreases. $\therefore T_d \propto I^2$

avoid this maintain constant frequency.

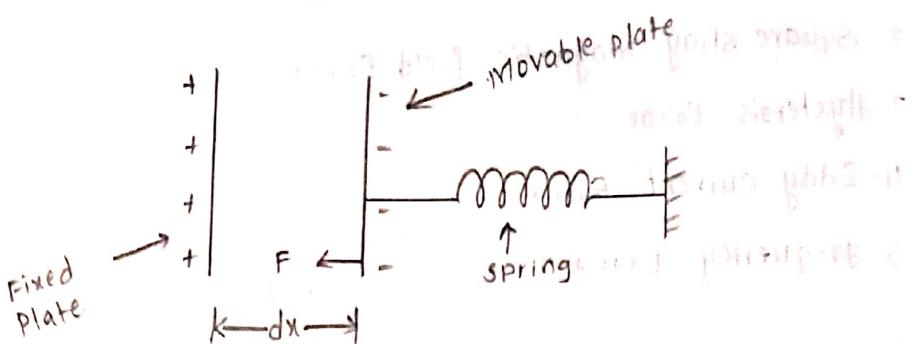Electrostatic Voltmeter → for measuring high voltage
It is used only for AC.



This type, working principle of this is based on electrostatic effect. It consists of two charged plates. One is fixed and the other one is movable plate. It works based on Electrostatic effect.. i.e., whenever two charged plates are brought nearer there exists force of attraction between them.

To provide controlling torque, spring control method is used.

Damping torque is provided by Air friction Damping.

\rightarrow Mechanical Work done = $F_x dx \rightarrow ①$

Let C = capacitance

~~Rec~~ $C = \text{capacitance}$ ~~discharge. The effect voltage of discharging will increase.~~

V = voltage

$\theta = \text{Reflection angle}$

Writing down the change in capacitance is difficult to understand

ΔV = change in voltage

$d\theta$ = change in reflection

→ change in current $i = \frac{dq}{dt} = \frac{d}{dt}[cv]$

$$\text{photons} = \dot{N} = C \frac{dv}{dT} + v \frac{dc}{dt} \rightarrow ②$$

→ Electrical Energy input = $\int v i dt$ (left) output (right)

$$= \int [C \frac{dv}{dt} + v \frac{dc}{dt}] dt$$

$$\therefore \text{Electrical Energy input} = cvdv + \frac{1}{2}v^2dc \rightarrow ③$$

→ Energy stored in a capacitor = $\frac{1}{2}cv^2$ which is increases

$$\text{to } \frac{1}{2}(c+dc)(v+dv)^2$$

→ change in stored energy = $\frac{1}{2}(c+dc)(v+dv)^2 - \frac{1}{2}cv^2$

$$\text{or capacitor ans} = \frac{1}{2}(c+dc)(v^2 + 2vdv + (dv)^2) - \frac{1}{2}cv^2$$

$$\begin{aligned} &= \frac{1}{2}cv^2 + cvdv + \frac{1}{2}cdv^2 + \frac{1}{2}v^2dc + vdvdc \\ &\quad + \frac{1}{2}dc(dv)^2 - \frac{1}{2}cv^2 \\ &\quad \text{neglect} \quad \text{neglect} \quad \text{neglect} \end{aligned}$$

$$\text{change in stored energy} = cvdv + vdvdc - \frac{1}{2}v^2dc \rightarrow ④$$

∴ Electrical Energy input = change in stored energy + Mechanical work done

$$cvdv + v^2 = \frac{1}{2}v^2dc + cvdv + F_x dx$$

$$\frac{1}{2}v^2dc = F_x dx$$

The linear motion is converted into a circular (or) Rotational

Hence, $F \rightarrow T_d$; $dx \rightarrow d\theta$

$$\therefore \frac{1}{2}v^2dc = T_d d\theta$$

$$\therefore T_d = \frac{1}{2}v^2 \frac{dc}{d\theta} \rightarrow ⑤$$

Reflecting torque = $T_d = \frac{1}{2}v^2 \frac{dc}{d\theta}$

\rightarrow controlling torque (T_c) = $K\theta \rightarrow ⑥$

At equilibrium, $T_d = T_c$

$$\frac{1}{2} V^2 \frac{dC}{d\theta} = K\theta$$

$$\therefore \text{Deflection}(\theta) = \frac{1}{2} \frac{V^2}{K} \frac{dC}{d\theta}$$

30/11/19

- Q1. An electrostatic voltmeter reading upto 2000 volts. It is controlled by a spring with a constant of 5×10^6 Nm/radians. has a full scale deflection 90 degree. The capacitance at zero voltage is 15 PF. what is capacitance when pointer indicates 2000 volts.

Sol: Given Data;

$$\text{Voltage} = 2000 \text{ Volts}$$

$$K_s = 5 \times 10^6 \text{ Nm/radians}$$

$$\theta = 90 \text{ degree}$$

$$C = 15 \text{ PF}$$

$$\pi/2 = 90^\circ$$

$$\theta = \frac{1}{2} \frac{V^2}{K} \frac{dC}{d\theta}$$

$$\frac{dC}{d\theta} = \frac{2 \times 5 \times 10^6 \times (\frac{\pi}{2})}{(2000)^2} \text{ C in radian}$$

$$\frac{dC}{d\theta} = 3.926 \text{ PF/radians}$$

To get only in "PF" without radians.


$$\text{Capacitance (C)} \rightarrow 0 - 2000 \text{ V} \Rightarrow 3.926 \times \frac{\pi}{2} \text{ PF}$$

$$\text{At } 2000 \text{ V, } C = 15 + 6.16 = 21.16 \text{ PF.} \quad = 6.16 \text{ PF}$$

Basic D.C Ammeter

for small winding, less current flows.

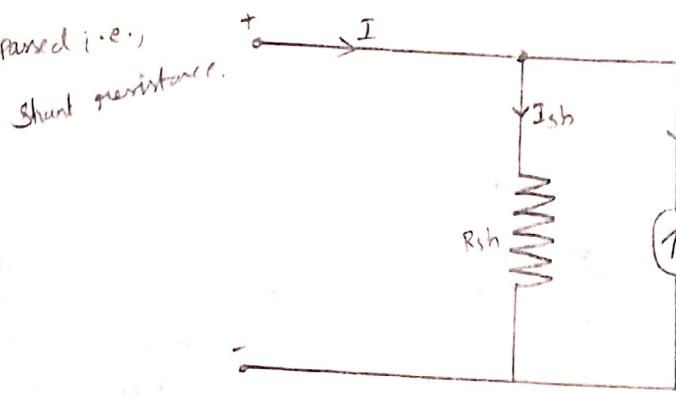for large currents, high amount of current should be bypassed i.e.,



Ammeter in series has

internal resistance in meter

more it connects to just p

more bulky, because high

current flows through

more resistance will be there

→ If voltmeter is

connected in parallel it has high voltage

drop

→ Let I_m = full scale deflection current

R_m = Internal resistance of coil/meter.

R_{sh} = Shunt resistance

I = Total current

I_{sh} = shunt current

→ voltage across both resistances must be same.

$$R_{sh} I_{sh} = I_m R_m$$

$$\therefore R_{sh} = \frac{I_m R_m}{I_{sh}}$$

from diagram, $I = I_{sh} + I_m$

$$\therefore I_{sh} = I - I_m \rightarrow ②$$

② in ①

$$R_{sh} = \frac{I_m R_m}{(I - I_m)} ; m = \frac{I}{I_m}$$

$$\therefore R_{sh} = \frac{R_m}{m-1}$$

Note: To increase the range of Ammeter "m" times, shunt required is " $\frac{1}{(m-1)}$ " times the meter resistance.

Q1 A 2mA meter with an internal resistance of 100 ohms is to be converted to 150mA ammeter. Calculate the value of shunt resistance required.

Sol: Given Data,

$$R_m = 100 \Omega$$

$$I_m = 2 \text{ mA}$$

$$I = 150 \text{ mA}$$

$$R_{sh} = ?$$


$$\therefore R_{sh} = \frac{I_m R_m}{I - I_m}$$

$$I_{sh} = I - I_m = 148 \text{ mA}$$

$$R_{sh} = \frac{2 \times 10^{-3} \times 100}{148 \times 10^{-3}}$$

$$\therefore R_{sh} = 1.35 \Omega$$

Multi Range Ammeter:

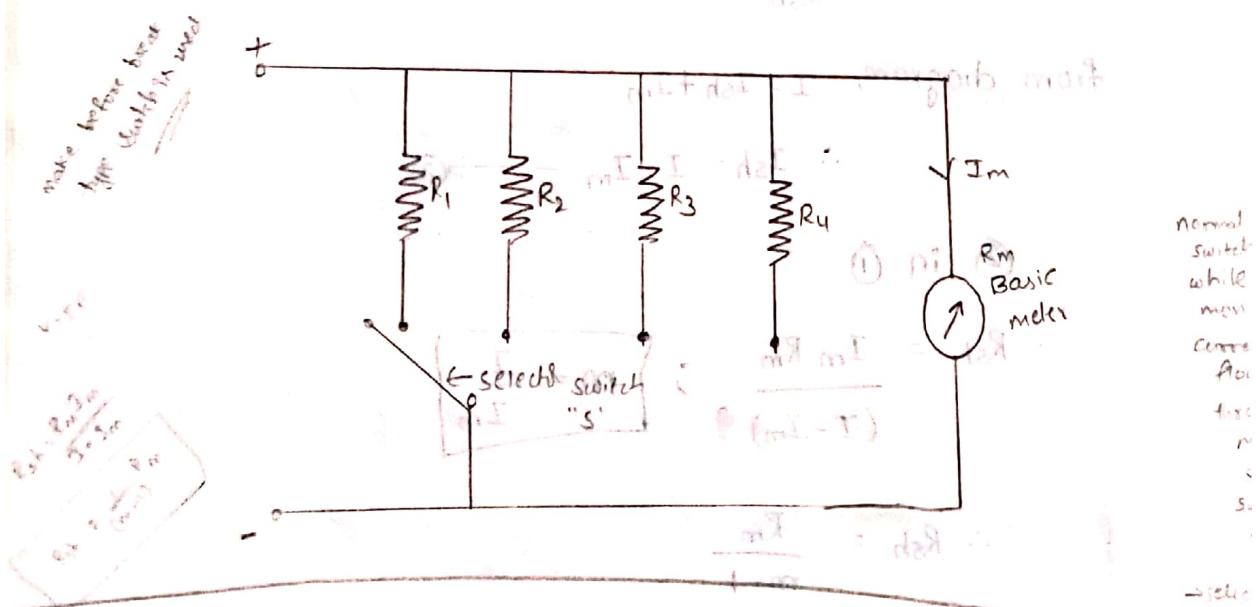

→ To consider accurate measurement, the working of each element is required. On selector switch, the operation of "S" on any resistance is done, by closing the resistance on which switch is existing, so that every element is calculated which is not present in terminal switch.

→ where R_1, R_2, R_3, R_4 are shunt resistances corresponding currents are I_1, I_2, I_3, I_4 respectively extending range

$$R_1 = \frac{R_m}{m_1 - 1} ; m_1 = \frac{I_1}{I_m}$$

$$R_2 = \frac{R_m}{m_2 - 1} ; m_2 = \frac{I_2}{I_m}$$


$$R_3 = \frac{R_m}{m_3 - 1} ; m_3 = \frac{I_3}{I_m}$$

$$R_4 = \frac{R_m}{m_4 - 1} ; m_4 = \frac{I_4}{I_m}$$

2/12/19 future better understand concept of shunt resistor

Design a multirange DC milliammeter with a basic meter having a resistance of 75Ω and full scale deflection for the current of 2mA . The required ranges are (0 to 10mA), (0 to 50mA) and (0 to 100mA).

Sol:

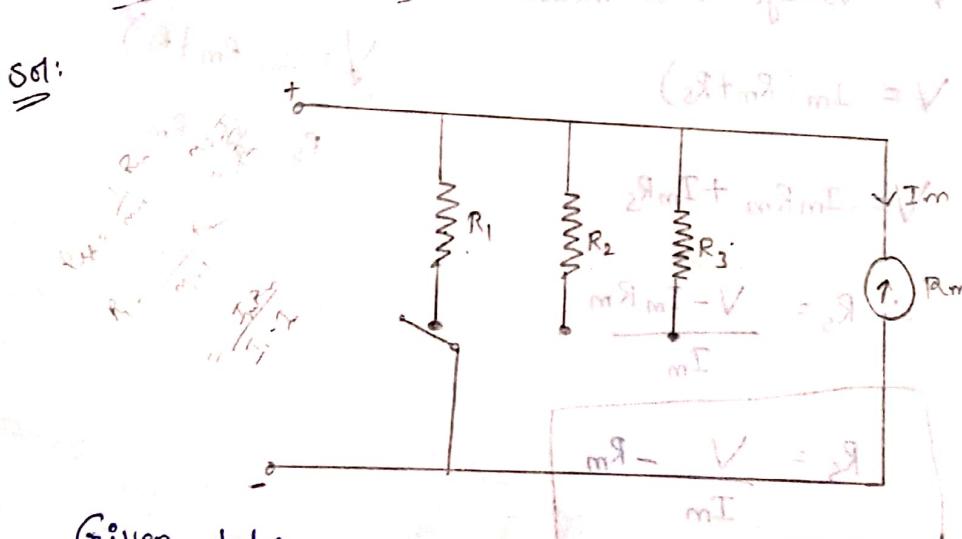

Given data,

$$R_m = 75\Omega$$

$$I_m = 2\text{mA}$$

$$\frac{V}{I} = \frac{R_m + R_{sh}}{I_m} = \frac{75 + R_{sh}}{2 \times 10^{-3}}$$

$$\rightarrow R_1 = \frac{I_m R_m}{I_1 - I_m} = \frac{2 \times 10^{-3} \times 75}{(10 - 2) \times 10^{-3}} = 18.75 \Omega$$

$$\rightarrow R_2 = \frac{I_m R_m}{I_2 - I_m} = \frac{2 \times 10^{-3} \times 75}{(50 - 2) \times 10^{-3}} = 3.125 \Omega$$


$$R_{sh} = \frac{I_m R_m}{I_1 - I_m}$$

$$R_{sh} = \frac{75 \times 2 \times 10^{-3}}{10 - 2} = 1.875 \Omega$$

$$m = \frac{I_1}{I_m}$$

$$\rightarrow R_3 = \frac{I_m R_m}{I_3 - I_m} = \frac{2 \times 10^3 \times 75}{(100 - 2) \times 10^3} = 1.530 \Omega$$

Basic DC Voltmeter

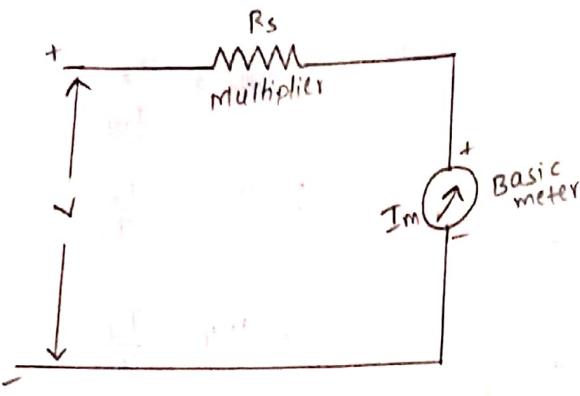

→ It consists of a series resistance called Multiplier.

and internal resistance of voltmeter is "R_m"

Let R_s = multimeter multiplier

R_m = Meter resistance

I_m = Full scale Deflection current

V = Voltage to be measured.

$$V = I_m (R_m + R_s)$$

$$V = I_m (R_m + R_s)$$

$$R_s = \frac{V - R_m}{I_m}$$

$$V = I_m R_m + I_m R_s$$

$$\therefore R_s = \frac{V - I_m R_m}{I_m}$$

$$R_s = \frac{V - R_m}{I_m}$$

→ m = multiplying power = $\frac{\text{Voltage to be measured}}{\text{Voltage drop across coil}} = \frac{V}{V_d}$

$$m = \frac{I_m R_m + I_m R_s}{I_m R_m}$$

$$m = 1 + \frac{R_s}{R_m}$$

$$1. R_s = (n-1) R_m$$

Q. A moving coil instrument gives a full scale deflection for a current of 20 mA with a potential difference of 200 mV across it.

if. calculate (i) shunt required to use it as an Ammeter

to get a range of $(0-200) \text{ mA}$.

(ii) Multiplier required to use it as a voltmeter

of range $(0-500) \text{ V}$.

$$I_m = 20 \text{ mA}$$

$$V_m = 200 \text{ mV}$$

Sol: Given data,

$$I_m = 20 \text{ mA} ; I = 200$$

$$V_m = 200 \text{ mV} = 2 \text{ mV} R_m$$

$$\therefore R_m = \frac{10}{20 + 10^3}$$

$$\therefore R_m = 10 \Omega$$

$$R_{sh} = \frac{I_m R_m}{I - I_m} = \frac{2 \times 10^3}{1 - 2 \times 10^{-3}}$$

$$V = 2mV + I_m R_m \\ R_S = \frac{V}{I_m} = \frac{200 \times 10^3 \times 10}{(200 - 20) \times 10^{-3}} = 10^5 \Omega \\ R_S = \frac{500}{20 \times 10^{-3}} = 10^5 \Omega \\ R_S = \frac{500}{20 \times 10^{-3}} = 25,000 \Omega \\ R_S = 25,000 \Omega \\ R_S = 25,000 \text{ k}\Omega$$

$$(i) R_{sh} = \frac{I_m R_m}{I - I_m} = \frac{20 \times 10^3 \times 10}{(200 - 20) \times 10^{-3}} = 1,000 \times 10^3 \Omega$$


$$(ii) R_s = \frac{V}{I_m} = \frac{500}{20 \times 10^{-3}} = 25,000 \Omega$$

V → $I_m R_m$
 R_s → $R_s + R_m$
 (Hence measured
voltage across
cell)

"2" to "notches" \rightarrow

$$\frac{2V}{10} + 19 = 20$$

MultiRange Voltmeter:-

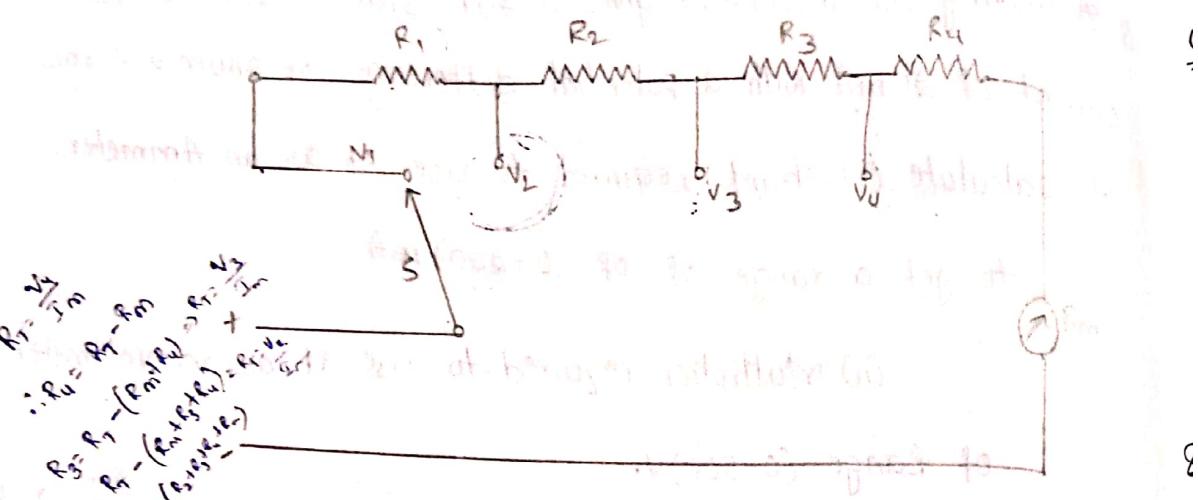

→ It consists of R_1, R_2, R_3 and R_4 are the multipliers connected in series.

→ The voltages V_1, V_2, V_3 & V_4 are the voltages corresponding to multipliers.

→ 4th position of "S":-

$$R_T = \frac{V_4}{I_m}$$

$$R_T = \frac{V_4}{I_m}$$

$$R_T = \frac{V_4}{I_m}$$

$$R_T = R_T - R_m$$

$$R_T = \frac{V_4}{I_m}$$

$$R_3 = R_T - (R_m + R_4)$$

$$R_3 = \frac{V_3}{I_m}$$

→ 3rd position of "S":-

$$R_T = \frac{V_3}{I_m} \quad R_T = \frac{V_3}{I_m} \quad R_3 = R_T - (R_m + R_4)$$

$$R_T = \frac{V_3}{I_m}$$

$$R_T = \frac{V_3}{I_m}$$

$$R_2 = R_T - (R_3 + R_m)$$

→ 2nd position of "S":

$$R_T = \frac{V_2}{I_m}$$

$$\therefore R_2 = R_T - (R_m + R_4 + R_3)$$

$$R_1 = R_T - (R_2 + R_3 + R_4)$$


→ 1st position of "S":

$$R_T = \frac{V_1}{I_m}$$


$$\therefore R_1 = R_T - (R_m + R_4 + R_3 + R_2)$$

Q: The basic D'Arsonval Galvanometer with an internal resistance of 50Ω & full scale deflection current of $2mA$ is used as a multirange voltmeter. Design a series string of multipliers to obtain the voltage ranges of $(0-10V)$; $(0-50V)$; $(0-100V)$ & $(0-500V)$.

$$R_m = 50\Omega \quad I_m = 2mA$$

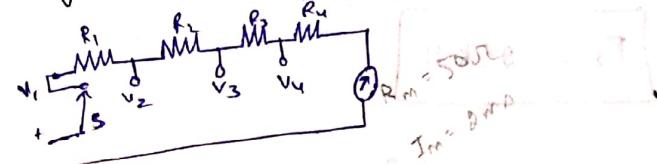

Sol:

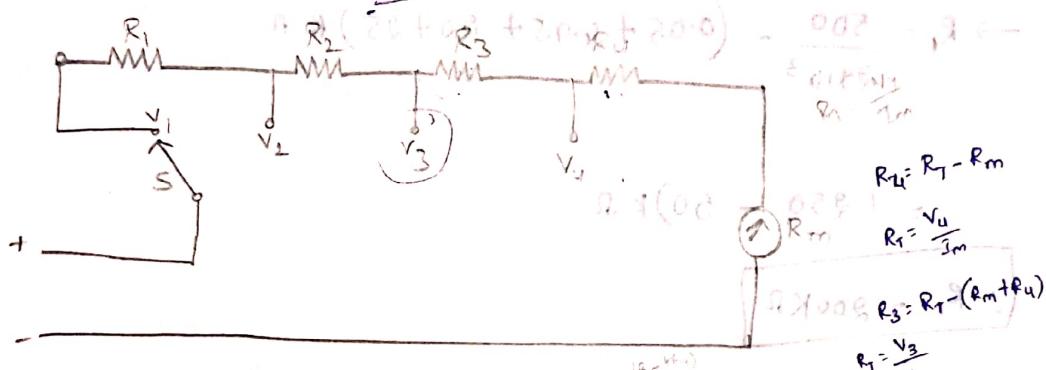

Given Data,

Internal Resistance (R_m) = 50Ω = $0.05K\Omega$

Full Scale Deflection Current (I_m) = $2mA$

$\therefore V_1 = (0-10)V$

4th position of S:

$$R_T = \frac{V_4}{I_m} = \frac{500}{2 \times 10^{-3}} = 250 \times 10^3 \Omega$$

$\therefore R_4 = R_T - R_m$

$$= 250 \times 10^3 - 50 = [5 - 0.05] K\Omega$$

$$R_4 = 4.95 K\Omega$$

3rd position:

$$R_3 = R_T - (R_m + R_4) =$$

$$= \frac{500}{2 \times 10^{-3}} - [5 - 0.05 + 4.95] \times 1000$$

$$= 25 K\Omega - 5 K\Omega$$

$$R_3 = 20 K\Omega$$

$$R_m + R_4 = mI \quad R_3 = R_T - (R_4 + R_m)$$

$$R_T = \frac{V_3}{I_m} = \frac{60}{2 \times 10^{-3}}$$

$$\frac{mI - I}{mI} = \frac{1000}{1000 + 1}$$

$$= \frac{0.1 \times 1000}{1000 + 1} =$$

$$\rightarrow R_2 = \frac{100}{2 \times 10^{-3}} - (0.05 + 4.95 + 20) \times 1000$$

$$= 50 \text{ k}\Omega - (25) \text{ k}\Omega$$

$$\boxed{R_2 = 25 \text{ k}\Omega}$$

$$\rightarrow R_1 = \frac{500}{2 \times 10^{-3}} - (0.05 + 4.95 + 20 + 25) \text{ k}\Omega$$

$$= (250 - 50) \text{ k}\Omega$$

$$\boxed{\therefore R_1 = 200 \text{ k}\Omega}$$

A moving coil instrument gives full scale deflection of 10 mA, when potential difference across its terminal is 100 mV; calculate

(i) shunt resistance for a full scale deflection corresponding to 100 A.

$$R_{sh} = ? \quad I = 100 \text{ A}$$

$$I_m = 10 \text{ mA}$$

$$V_m = 100 \text{ mV}$$

$$R_m = \frac{V_m}{I_m} = \frac{100 \text{ mV}}{10 \text{ mA}} = 10 \text{ }\Omega$$

$$R_{sh} = \frac{I_m R_m}{I - I_m} = \frac{10 \text{ mA} \times 10 \text{ }\Omega}{100 \text{ A} - 10 \text{ mA}} = \frac{10 \times 10^{-3} \text{ A} \times 10 \text{ }\Omega}{100 \text{ A} - 10 \text{ mA}}$$

(ii) The series resistance for a full scale reading of 1000 V.

(iii) The power dissipation in each case.

Sol: Given Data,

$$I_m = 10 \text{ mA}$$

$$V = I_m R_m = 100 \text{ mV}$$

$$1000 \text{ V} = I_m R_m + I_m R_s$$

$$(i) R_{sh} = \frac{I_m R_m}{I - I_m}$$

$$= \frac{100 \times 10^{-3} \times 10}{100 - 0.01} = 1.000 \times 10^{-3}$$

$$R_{sh} = 1 \text{ m}\Omega \Rightarrow 1.000 \times 10^{-3} \text{ }\Omega$$

$$(i) R_s = \frac{V}{I_m} - R_m$$

$$= \frac{1000}{10 \times 10^{-3}} = 100000 \Omega$$

$$\boxed{R_s = 99,990 \Omega}$$

$$(iii) \text{ power Dissipation} = I^2 R_{sh}$$

$$(i) = (100)^2 \times 1.0001416^{-3} = 10.001416 \text{ W}$$

$$\boxed{P = 10.001 \text{ W}}$$


$$(ii) P = \frac{V^2}{R_s}$$

$$= (100)^2 / (99,990)$$

$$\boxed{P = 10.001 \text{ W}}$$

Design a multirange ammeter with ranges of 1A, 5A, 25A & 125A.
A D'Arsonval Galvanometer with internal resistance of 730Ω & full scale current of 5mA.

So:

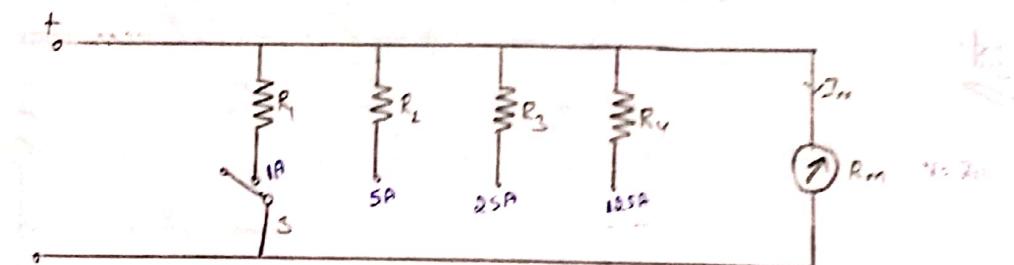

$$\rightarrow R_1 = \frac{R_m}{m_1 - 1}$$

$$m_1 = \frac{I_1}{I_m} = \frac{1}{5 \times 10^{-3}} = 200$$

$$\therefore R_1 = \frac{730}{200 - 1} = 3.668 \Omega$$

$$\rightarrow R_2 = \frac{R_m}{m_2 - 1}$$

$$m_2 = \frac{I_2}{I_m} = \frac{5}{5 \times 10^{-3}} = 1000$$

when "S" is at R_1
all resistances are considered
which has high current
resistance
so less current flows i.e., 1A

$$R_1 = \frac{730}{200 - 1} \Omega$$

$$\rightarrow R_2 = \frac{730}{1000-1} = 0.7307 \Omega$$

$$\rightarrow R_3 = \frac{R_m}{m_3-1} ; m_3 = \frac{I_3}{I_m} = \frac{25}{5 \times 10^{-3}} = 5000$$

$$\therefore R_3 = \frac{730}{5000-1} = 0.1460 \Omega$$

$$\rightarrow R_4 = \frac{R_m}{m_4-1} ; m_4 = \frac{I_4}{I_m} = \frac{125}{5 \times 10^{-3}} = 25,000$$


$$\therefore R_4 = 0.0292 \Omega$$

$$[0.146 + 0.0292]$$

A Basic D'Arsonval Galvanometer with full scale reading of

50mA and an internal resistance of 1800Ω is to be

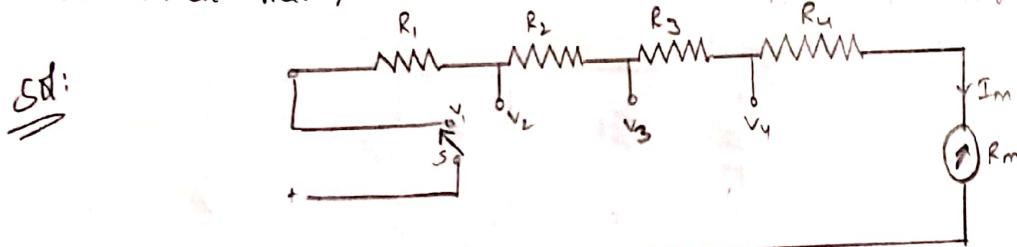converted into (0-1)V, (0-5)V, (0-25)V; (0-125)V. Multirange voltmeter using individual multipliers. calculate the values of individual multipliers.



→ 4th position of "S"

$$R_4 = R_T - R_m \quad [\because R_T = \frac{V_4}{I_m} = \frac{1}{50 \times 10^{-3}}]$$

$$= 20,000 - 1800$$

$$= 18,200 \Omega$$

→ 3rd position of "S"

$$R_3 = R_T - (R_m + R_4) \quad [\because R_T = \frac{V_3}{I_m} = \frac{5}{50 \times 10^{-3}} = 100,000]$$

$$= 100,000 - (1800 + 18,200)$$

$$R_3 = 80,000 \Omega$$

→ 2nd position of "S"

= ~~the load is connected and no current flowing through load~~ →

$$R_2 = R_T - (R_m + R_3 + R_u) \quad [\because R_T = \frac{V_2}{I_m} = \frac{25}{5 \times 10^{-6}} = 5 \times 10^5]$$

$$= 500,000 - (1800 + 18,200 + 80,000)$$

→ ~~and hence current passing through load is zero~~

$$R_2 = 4,00,000 \Omega$$

→ 1st position of "S"

$$R_1 = R_T - (R_m + R_3 + R_u + R_2) \quad [\because R_T = \frac{V_1}{I_m} = \frac{50}{5 \times 10^{-6}} = 10 \times 10^5]$$

$$= 10 \times 10^5 - 5 \times 10^5$$

→ ~~same current passing through~~

$$\frac{R_1}{V} = \frac{10 \times 10^5}{50 \times 10^5} \text{ A} \Rightarrow \text{if } \frac{1}{50} = (2) \text{ division}$$

$$R_1 = 2 M\Omega$$

~~same current passing through 2nd division~~

~~is division to connect 2nd division of voltmeter~~

precautions to be taken for an Ammeter :-

→ polarities must be observed correctly. otherwise, it leads to ~~mechanical damage~~ → negative mechanical work, which damages the instrument.

→ Ammeter consists low resistance, hence it must be connected in series with the ~~circuit~~ $\rightarrow R_2 = 0$

→ while using multirange ammeters, highest range is measured and going on low values are measure.

3/12/19 precautions to be taken for Voltmeter :-

→ As the resistance of voltmeter is high, it must be connected across ~~or~~ parallel to circuit.

→ polarities must be observed correctly.

→ in multirange voltmeter, first take highest voltage range

and then lowest.

Requirements of shunt & Multiplier:-

- shunt & multiplier must be low temperature coefficient.
- Either Manganine (or) constantan are used while designing.
- while soldering, it doesn't produce any thermal effect esp's

Sensitivity :- [S]

$S = \frac{R_m}{I_m}$ It is defined as the ratio of total resistance to the voltage range. remains same.

$$\text{Sensitivity } (S) = \frac{1}{I_m} \text{ n/V } (8) \text{ k}\Omega/\text{V}$$

$$(18) S = \frac{R_T}{V}$$

$$R_T = \frac{V}{I_m}$$

$$2m = \frac{V}{R_T}$$

$$\frac{1}{2m} = \frac{R_T}{V}$$

example:- R_1, R_2, R_3, R_4 are multipliers ; V_1, V_2, V_3, V_4 are corresponding voltages, the multipliers in terms of sensitivity is

$$R_4 = SV_4 - R_m \quad [\because S = \frac{1}{I_m}]$$

$$R_4 = R_T - R_m$$

$$R_T = \frac{V_4}{I_m}$$

$$\therefore R_4 = SV_4 - R_m$$

$$R_3 = SV_3 - (R_m + R_4)$$

$$R_3 = R_T - (R_m + R_4)$$


$$R_2 = SV_2 - (R_m + R_4 + R_3)$$

$$R_2 = R_T - (R_m + R_4 + R_3)$$

$$R_1 = SV_1 - (R_m + R_4 + R_3 + R_2)$$

$$R_1 = R_T - (R_m + R_4 + R_3 + R_2)$$

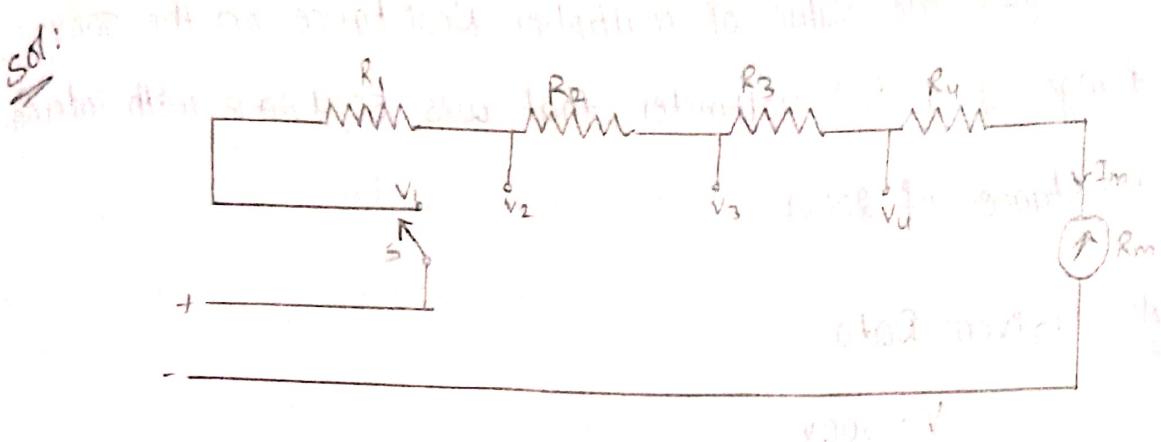- ① The Basic "D'Arsonval" Galvanometer with an internal resistance of 50Ω & full scale deflection current of $2mA$ is used as multi range voltmeter. Design the spring of multipliers to obtain $(0-10)V$; $(0-50)V$; $(0-100)V$; $(0-500)V$ in terms of sensitivity.



$$\rightarrow \text{Sensitivity } (S) = \frac{1}{I_m} = \frac{1}{2 \times 10^{-3}} = 500 \Omega/V$$

At 4th position:

$$R_4 = (0.07) 500 \Omega = 3.5 \Omega$$

$$R_4 = SV_4 - R_m$$

$$= 500(10) - 50$$

$$R_4 = 4950 \Omega$$

$$R_4 = 4.950 k\Omega$$

At 3rd position:-

$$R_3 = SV_3 - (R_m + R_4)$$

$$= 500(50) - (50 + 4950)$$

$$= 20,000 \Omega$$

$$R_3 = 20 k\Omega$$

At 2nd position:-

$$R_2 = SV_2 - (R_m + R_4 + R_3)$$

$$= 500(100) - (50 + 4950 + 20,000)$$

$$= 25000 \Omega$$

$$R_2 = 25 k\Omega$$

At 1st position:-

$$R_1 = SV_1 - (R_m + R_4 + R_3 + R_2)$$

$$= 500(500) - (50 + 4950 + 20,000 + 25000)$$

$$R_1 = 400 k\Omega$$

Q) Calculate the value of multiplier Resistance on the 500V range of a DC voltmeter that uses 50 μ Amp with internal resistance of 200 Ω .

Sol: Given Data,

$$V = 500V$$

$$I_m = 50\mu A$$

$$R_m = 200\Omega$$

$$\therefore R_s = \frac{V}{I_m} - R_m$$

$$= \frac{500}{50 \times 10^{-6}} - 200$$

$$R_s = 9999800 \Omega$$

$$R_s = 9.9998 M\Omega \quad (or) \quad 9999.8 k\Omega$$

Q) The meter "A" has a range of (0-100)V & multiplier resistance of 25k Ω . Meter "B" has a range of (0-1000)V and multiplier resistance of 150k Ω . Both meters has basic resistance of 1k Ω . Which meter is more sensitive.

Sol:

$$WKT, R = SV - (R_m + R_s)$$

$$\rightarrow R_A = SVA - R_m$$

$$25 \times 10^3 = S(100) - (1 \times 10^3)$$

$$S_A = 260 \Omega/V$$

$$R_B = SV_B - R_m$$

$$150 \times 10^3 = S(1000) - (1000)$$

$$S = 151 \Omega/V$$

Here, Meter "A" is a high value. Therefore Meter "A" is more sensitive than Meter "B".

4/12/19

up measured high & fast

Instrument Transformers:-


To measure high range of currents & voltages

Instrument Transformers are used.

① current Transformer [C.T]

② Potential Transformer [P.T]

① Current Transformer:-

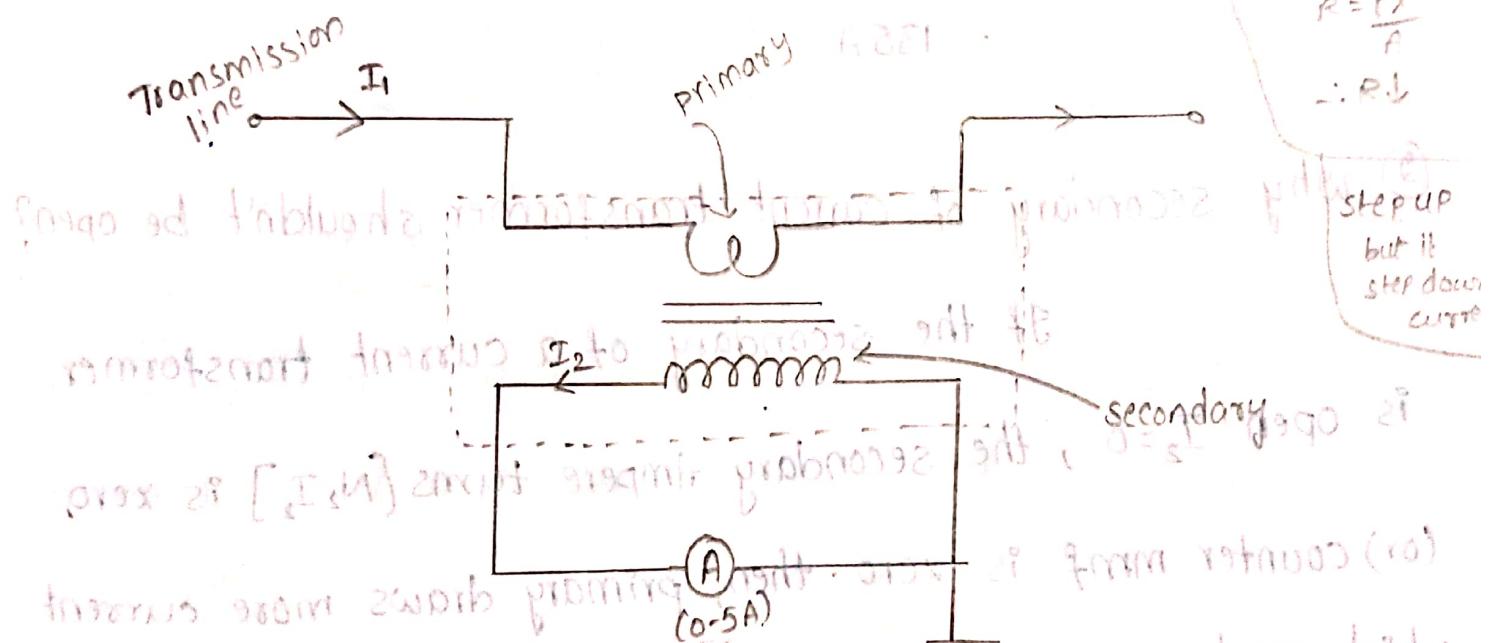

where,

I_1 = primary current

I_2 = secondary current

N_1 = Number of primary turns

N_2 = Secondary winding turns

$$\frac{I_1}{I_2} = \frac{N_2}{N_1}$$

if $I_2 = 0$, count 1 mm
then high primary current
high flux, higher
which increases heat
temp. T/F burns out
Remedy: Ammeter is
used (F) ground

Example:

- ① A 250:5 current transformer is used along with an ammeter. If ammeter reading is 2.7 Amp. Estimate line current.

Sol:

$$\frac{I_1}{I_2} = \frac{N_2}{N_1}$$

$$\frac{I_1}{2.7} = \frac{250}{S}$$

$$I_1 = 2.7 \times \frac{250}{S}$$


$$= 135 \text{ A}$$

- ② Why secondary of current transformer shouldn't be open?

If the secondary of a current transformer is open $I_2 = 0$, the secondary ampere turns [$N_2 I_2$] is zero (or) counter mmf is zero. Then, primary draws more current which produces more flux in core, so induces more emf in secondary, heat will be dissipated more which causes rise of temperature and transformer may be burn out. If it is very dangerous from operator's point of view.

Note:- Secondary of current transformer should be connected with Ammeter (or) grounded with low resistance.

Potential Transformer: — [P.T]

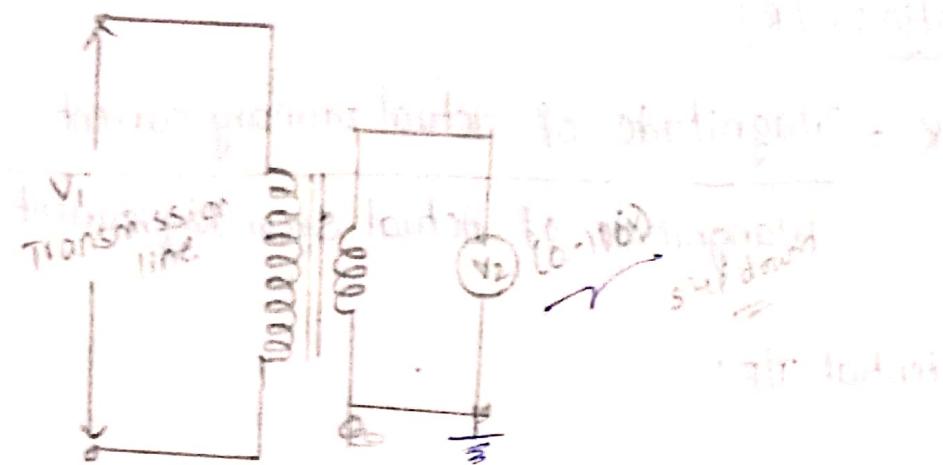

where, N_2 = secondary no. of turns
 N_1 = primary no. of turns

V_1 = Primary voltage

V_2 = Secondary voltage

$$\frac{V_2}{V_1} = \frac{N_2}{N_1}$$

example:

A $11000 : 110$ V potential transformer is used along-with an voltmeter. If voltmeter reading is 87.5 V. Estimate line voltage.

sol:

$$\frac{N_2}{N_1} = \frac{V_2}{V_1}$$

$$V_1 = V_2 \times \frac{N_1}{N_2}$$

$$= 87.5 \times \frac{11000}{110}$$

$$(a) = \frac{11000 + 57.5}{110} = 1000$$

$$= 8750$$

other problem $\frac{11000}{11000} = 10.00$

$$\frac{11000}{11000} = 0.875 \Rightarrow 8750$$

Ratios in Instrument Transformers :-

① Actual Ratio :- [R]

$$R = \frac{\text{Magnitude of Actual primary current}}{\text{Magnitude of Actual secondary current}}$$

for CT


for potential T/F :-

$$R = \frac{\text{Magnitude of Actual primary voltage}}{\text{Magnitude of Actual secondary voltage}}$$


5/12/19

② Nominal Ratio :- [k_n]
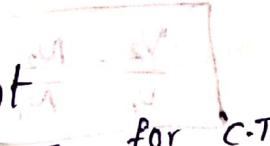
$$k_n = \frac{\text{Rated primary current}}{\text{Rated secondary current}}$$



for C.T

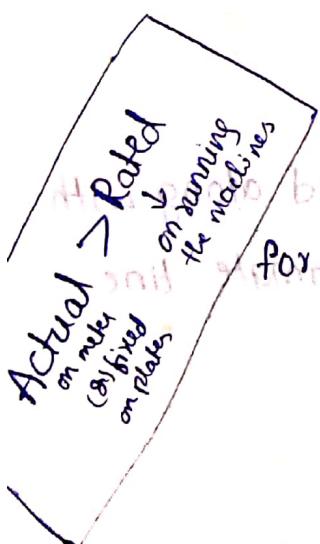

for potential T/F :-

$$k_n = \frac{\text{Rated primary voltage}}{\text{Rated secondary voltage}}$$

$$= \frac{220}{11} = 20$$

③ Turns Ratio :- [n]

$$n = \frac{\text{No. of turns in secondary wdg}}{\text{No. of turns in primary wdg}}$$

for C.T

for potential T/F :-

$$n = \frac{\text{No. of turns in primary wdg}}{\text{No. of turns in secondary wdg}}$$

④ Ratio of correction factor :—

It is defined as actual ratio to the nominal ratio.

$$\text{Ratio of correction factor} = \frac{R}{k_n}$$

$$\therefore R = \text{Ratio of correction factor} \times k_n$$

⑤ Total Burden of secondary winding :—

$$\text{Total Burden of } 2^\circ \text{ wdg} = \frac{\text{secondary induced voltage square}}{\text{impedance due to } 2^\circ \text{ wdg \& load}}$$

$$= \frac{V^2}{Z_S + Z_L} \xrightarrow{\text{[potential T/F]}} (or)$$

$$= I_s^2 [Z_S + Z_L] \xrightarrow{\text{[current T/F]}}$$

$$= \text{secondary current square} \times \text{Total impedance due to } 2^\circ \text{ wdg \& load.}$$


$$(ii) \text{ Secondary Burden due to load} = \frac{\text{secondary induced voltage square}}{\text{impedance due to load}}$$

(8)

$$= \text{secondary current square} \times \text{impedance due to load}$$

$$\text{i.e., } \frac{V^2}{Z_L} \quad (8) \quad I_s^2 Z_L$$

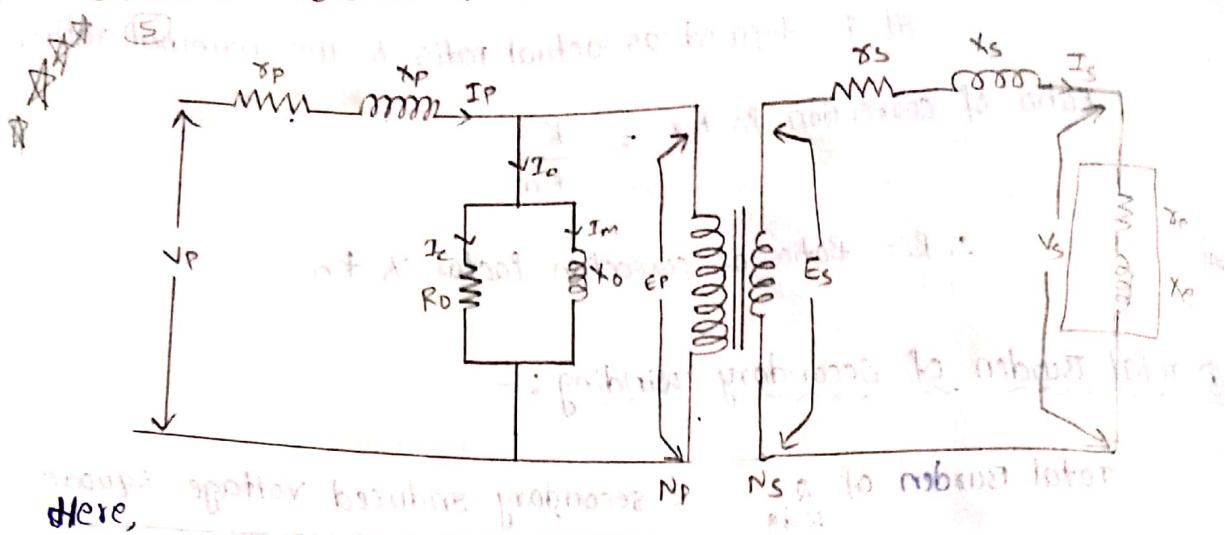Equivalent circuit of a current transformer



Here, τ_p = primary leakage reactance per phase N_p

here V_p = primary voltage

τ_p = primary resistance

χ_p = " reactance"

I_p = " current"

I_0 = No load current

at sub side τ_s = sub leakage reactance per phase

χ_s = core component of current

I_m = Magnetising current

here τ_s = sub leakage reactance per phase

τ_s = No load resistance

χ_s = No load reactance

E_p = Primary induced Emf

N_p = primary no. of turns

E_s = Secondary induced Emf

N_s = Secondary no. of turns

τ_s = Secondary resistance

χ_s = " reactance"

I_s = " current"

V_s = " voltage"

τ_e = Load resistance

χ_e = Load reactance



$\rightarrow \text{current } I_p = (I_o + ab) + (bc)$
 $\rightarrow ab = I_o \cos(\delta + \alpha)$ & $bc = I_o \sin(\delta + \alpha)$
 $\rightarrow ab + bc = I_o \cos(\delta + \alpha) + I_o \sin(\delta + \alpha)$ consider small angle
 $\rightarrow ab + bc = I_o (\cos(\delta + \alpha) + \sin(\delta + \alpha))$


Consider $\triangle bac$,

$$\rightarrow \sin(90 - \delta - \alpha) = \frac{bc}{ac}; ac = I_o, ad = nI_s, oc = I_p$$

$$\sin[90^\circ(\delta + \alpha)] = \frac{bc}{ac}$$

$$\cos(\delta + \alpha) = \frac{bc}{ac}$$
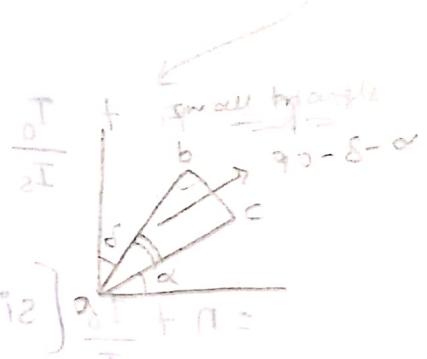
$$\therefore bc = I_o \cos(\delta + \alpha)$$



$$[\sin(90^\circ(\delta + \alpha)) + \cos(90^\circ(\delta + \alpha))]^2$$

$$\rightarrow 1 \rightarrow \textcircled{1} \frac{\pi + 2n\pi + \alpha}{2\pi} + \pi = 2$$

$$\rightarrow \cos(90 - \delta - \alpha) = \frac{ab}{ac}$$

$$\therefore ab = I_o \sin(\delta + \alpha)$$

→ Snipperle 3v+ = 2 results

large triangle
consider I_{obc}

$$(oc)^2 = (ob)^2 + (bc)^2$$

$$(oc)^2 = (oa+ab)^2 + (bc)^2$$

$$I_p^2 = (nI_s + I_o \sin(\delta+\alpha))^2 + (I_o \cos(\delta+\alpha))^2$$

$$I_p^2 = n^2 I_s^2 + 2nI_s I_o \sin(\delta+\alpha) + I_o^2 \sin^2(\delta+\alpha) + I_o^2 \cos^2(\delta+\alpha)$$

$$I_p^2 = n^2 I_s^2 + 2nI_s I_o \sin(\delta+\alpha) + I_o^2$$

Here, I_o^2 is modified as $I_o^2 \sin^2(\delta+\alpha)$ [$\because \sin(\delta+\alpha) \ll I_o$]

since less value it doesn't have any impact

$$I_p^2 = n^2 I_s^2 + 2nI_s I_o \sin(\delta+\alpha) + I_o^2 \sin^2(\delta+\alpha)$$

$\left[\because a^2 + 2ab + b^2 = (a+b)^2 \right]$

$$\therefore I_p = nI_s + I_o \sin(\delta+\alpha) \rightarrow ③$$

$$\rightarrow \text{Actual Ratio}(R) = \frac{I_p}{I_s} = \frac{nI_s + I_o \sin(\delta+\alpha)}{I_s}$$

From parallelogram (I_m, I_o, I_c)

$$\cos \alpha = \frac{I_m}{I_o}$$

$$I_m = I_o \cos \alpha$$

$$\sin \alpha = \frac{I_c}{I_o}$$

$$I_c = I_o \sin \alpha$$

$$\therefore R = n + \frac{I_o}{I_s} \sin(\delta+\alpha) \quad \text{for } \delta = 30^\circ : \frac{\partial d}{\partial \delta} = (\omega - 2 - \omega P) \text{ rad}$$

$$= n + \frac{I_o}{I_s} [\sin f \cos \alpha + \cos f \sin \alpha] \quad \left[\because \sin(A+B) = \sin A \cos B + \cos A \sin B \right]$$

$$R = n + \frac{I_m \sin f + I_c \cos f}{I_s}$$

where $f = +ve \rightarrow \text{lagging pf}$

$f = -ve \rightarrow \text{leading pf}$

$$\frac{\partial d}{\partial \delta} = (\omega - \omega_P - \omega_m \cos \delta) \quad I_m = I_o \cos \delta$$

$$\frac{\partial d}{\partial \delta} = (\omega - \omega_P - \omega_m \sin \delta) \quad I_c = I_o \sin \delta$$

(ii) Phase angle "θ":-

Consider Δ_{abc} ,

$$\tan \theta = \frac{bc}{ab} = \frac{bc}{oa+ab} = \frac{I_o \cos(\delta+\alpha)}{nI_s + I_o \sin(\delta+\alpha)}$$

$$\tan \theta \approx 0 = \frac{I_o \cos(\delta+\alpha)}{nI_s} \quad [\text{Here, Neglect } I_o \sin(\delta+\alpha)]$$

$$\theta = \frac{I_o}{nI_s} [\cos \delta \cos \alpha - \sin \delta \sin \alpha]$$

* $\theta = \frac{Im \cos \delta - I_c \sin \delta}{nI_s}$ * radians $I_c = I_o \sin \delta$
 based on $\tan \theta = \frac{\text{opposite}}{\text{adjacent}}$ $Im = I_o \cos \delta$

$\therefore \theta = \frac{180}{\pi} \left[\frac{Im \cos \delta - I_c \sin \delta}{nI_s} \right]$ degree

Approximate Results:-

In practical $\delta = 0^\circ$; $\sin \delta = 0$; $\cos \delta = 1$

$$R = n + \frac{I_c}{I_s}; \quad \theta = \frac{180}{\pi} \frac{Im}{nI_s} \text{ degrees}$$

Errors in current Transformers:-

There are two types of errors

① Ratio error

② Phase Angle error.

① Ratio error :- $\left(\frac{n_s}{n_p} \right) \frac{0.81}{0.99} = 0.01$ (ii)

$$\frac{I_s}{I_p} + \alpha = 1 + 0.01 = 1.01$$

In practical, the ratio $\frac{N_s}{N_p} = \frac{I_p}{I_s}$ are not equal.

Hence the errors are produced. These errors are called Ratio error.

$$\% \text{ error} = \frac{\text{Nominal ratio} - \text{Actual ratio}}{\text{Actual ratio}} \times 100$$

$$\% \text{ Error} = \frac{k_n - R}{R} \times 100$$

② Phase angle error: In practice, the phase angle difference between E_p & E_s is not 180° i.e., $\angle 180^\circ$. Hence, the errors are produced is called phase angle error.

$$\theta = \frac{180}{\pi} \left[\frac{I_m \cos \delta - I_c \sin \delta}{n I_s} \right]$$

Example: A current T/F with 5 primary turns has no load

Components are magnetising component = 102 A ; core loss component = 38 A , current T/F ratio is $\frac{1000}{5}$. Calculate the

Approximate ratio error at full load.

Sol: Given Data,

Current T/F

$$\text{Magnetising } I_m = I_o \cos \alpha = 102 \text{ A}$$

$$\text{core loss comp } I_c = I_o \sin \alpha = 38 \text{ A}$$

$$I_m = 102 \text{ A}$$

$$\frac{I_1}{I_2} = \frac{N_2}{N_1}$$

$$\frac{I_1}{I_2} = \frac{1000}{5}$$

$$\frac{I_1}{I_2} = 200$$

Approximate results:-

$$(i) R = n + \frac{I_c}{I_s}$$

$$(ii) \theta = \frac{180}{\pi} \left[\frac{I_m}{n I_s} \right]$$

$$= 200 + \frac{38}{5} = \frac{211}{5} = 42.2 \text{ ohms}$$

$$\text{error} = \frac{180}{\pi} \left[\frac{102}{200 \times 5} \right] = 5.8^\circ$$

$$R = 207.6$$

$$\therefore \text{Ratio error} = \frac{k_n - R}{R} \times 100$$

Here, $k_n = \frac{I_p}{I_s} = 800$

$$= \frac{800 - 207.6}{207.6} \times 100$$

$$\therefore \text{Error} = -3.66 \%$$

A current TIF has a single turn primary & 400 secondary turns. The magnetising current is 90A while coreloss current is 40Amps Secondary circuit phase angle $\phi_S = 28^\circ$. calculate the Actual primary current & ratio error when secondary carries 5Amp current.

Sol: Given,

$$N_p = 1 ; N_s = 400$$

$$I_m = 90 \text{ A} ; I_c = 40 \text{ A}$$

$$I_s = 5 \text{ Amp}$$

$$S = 28^\circ$$

Find:- Actual primary current = ?

ratio errors = ?

$$\text{Ratio error} = \frac{k_n - R}{R} \times 100$$

$$\rightarrow R = n + \frac{I_m \sin S + I_c \cos S}{I_s}$$

$$= 400 + \frac{[90(0.469)] + [40(0.882)]}{5}$$

$$R = 415.498$$

$$\rightarrow R = \frac{\text{Actual Primary current}}{\text{Actual secondary current}}$$

$$N_p = 1 ; N_s = 400$$

$$I_m = 90 \text{ A} = I_o \cos \delta$$

$$I_c = 40 \text{ A} = I_o \sin \delta$$

$$\delta = ?$$

$$I_o = \frac{K_n - R}{R} \times 100$$

$$K_n = \frac{I_p}{I_s}$$

$$n = \frac{I_p}{I_s} = \frac{N_s}{N_p} = \frac{400}{1}$$

$$n = 400$$

$$S = 28^\circ$$

$$\sin(28^\circ) = 0.469$$

$$\cos(28^\circ) = 0.882$$

$$k_n = \frac{I_p}{I_s}$$

$$n = \frac{I_p}{I_s}$$

$$I_p = 400 \times 5$$

$$I_p = 2000 \text{ A}$$

$$\rightarrow n = \frac{I_p}{I_s}$$

$$I_p = n I_s$$

$$= 400 \times 5$$

$$I_p = 2000 \text{ A}$$

$$\rightarrow K_n = \frac{\text{Rated primary current}}{\text{Rated secondary current}} = \frac{2000}{5}$$

$$K_n = 400$$


→ Ratio error:

$$= \frac{400 - 415.498}{415.498} \times 100$$

$$\text{Ratio error} = -3.814 \%$$

9/12/19

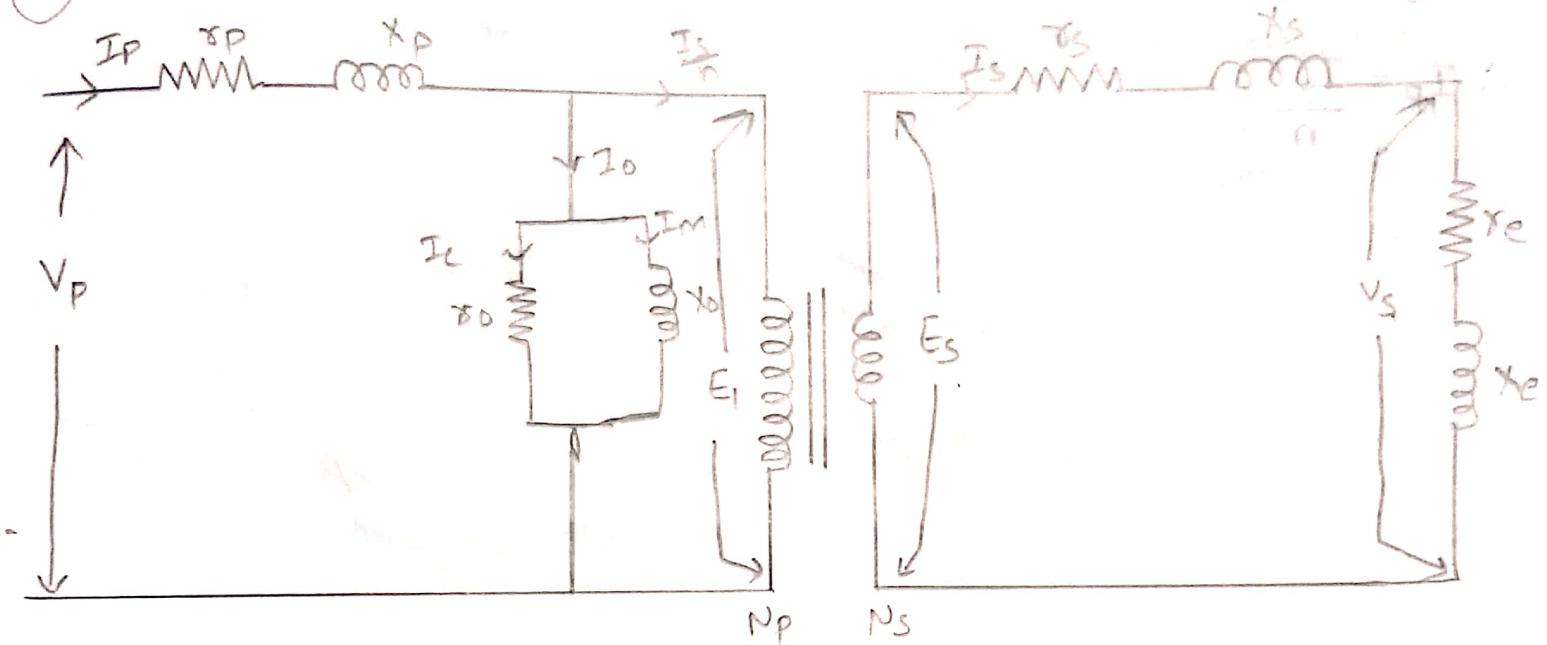⑥ Equivalent circuit of potential Transformer :-



where Terms explanation .

where, Terms explanation.

V_p = Primary voltage

I_p = Primary current

r_p = Primary resistance

x_p = Primary reactance

I_0 = No load current

I_c = core component of current

I_m = Magnetising current

r_0 = No load resistance

x_0 = No load reactance

E_i = primary induced emf

N_p = primary no. of turns

N_s = secondary no. of turns

E_s = secondary induced emf

r_s = secondary resistance

x_s = secondary reactance

V_s = secondary voltage

r_e = load resistance


x_e = load reactance.

According to potential T/F,


$$n = \frac{N_p}{N_s} = \frac{V_p}{V_s} = \frac{I_s}{I_p}$$

$$E_p = V_o + I_o R_o + I_o Z_o$$

$$\therefore I_p = \frac{I_s}{n}$$

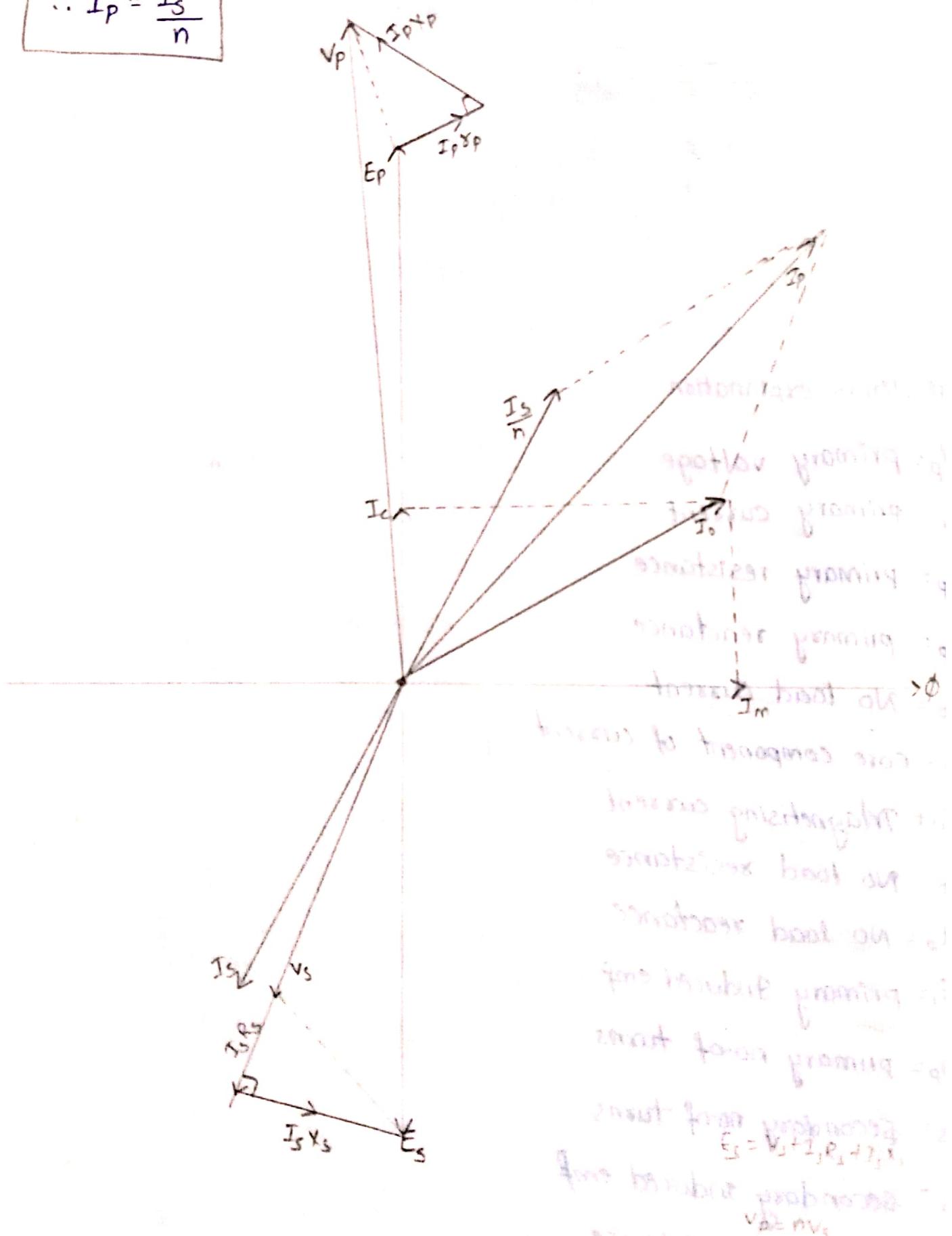

secondary are transferred to primary.

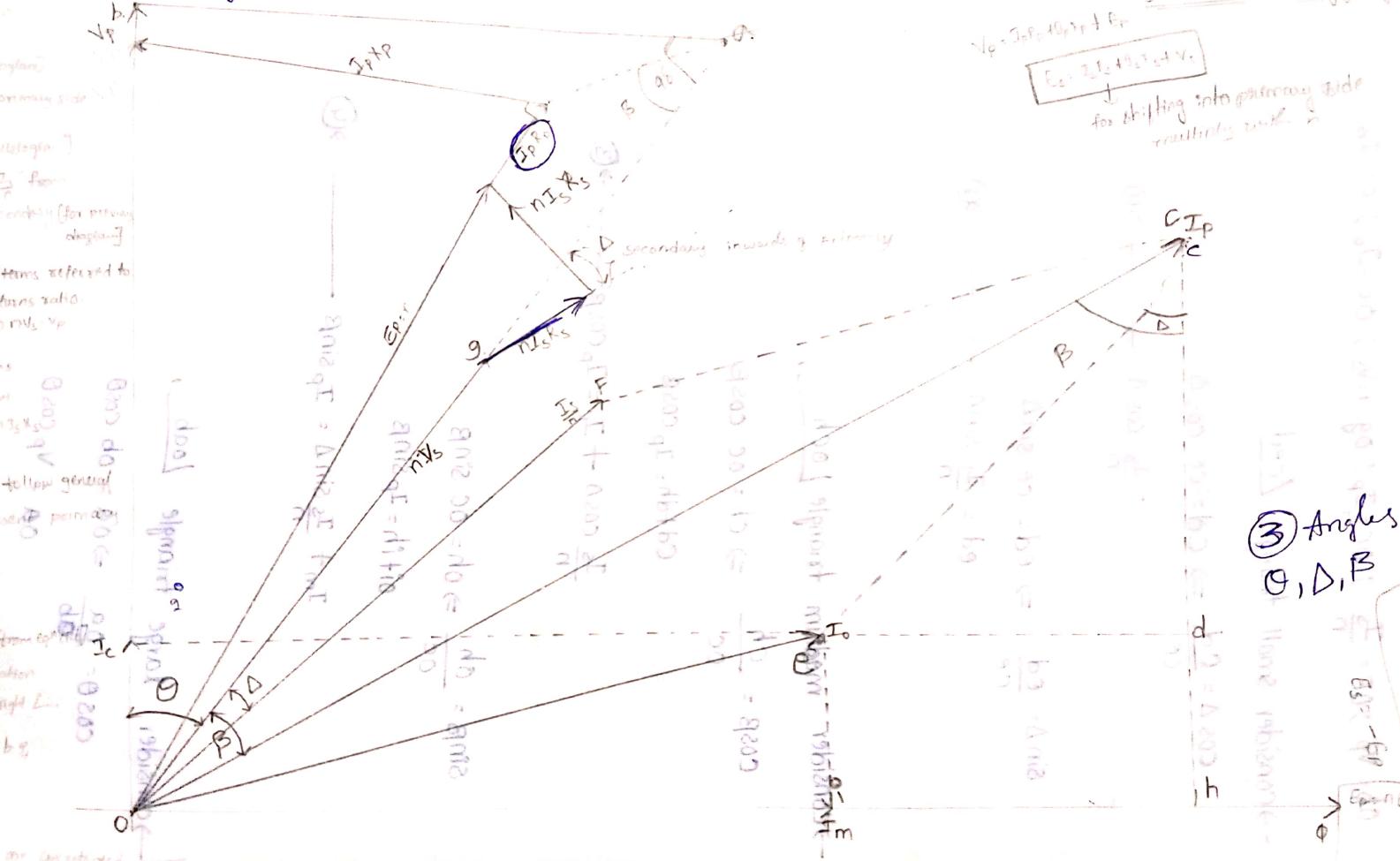

From Diagram,

From Diagram, $ce = \frac{I_b}{n}$

$$ob = v_p; OF = \frac{I_s}{n}; OC = I_p; OG = nV_s; OE = I_o; Oi = I_m$$

→ consider small triangle Iced

$$\cos A = \frac{cd}{ce} \Rightarrow cd = ce \cos A \\ = \frac{I_s}{n} \cos A \quad \longrightarrow \textcircled{1}$$

$$\sin D = \frac{ed}{ce} \Rightarrow ed = ce \sin D$$

(2)

$$ed = \frac{Is}{n} \sin D$$

→ consider medium triangle Loch,

$$\cos\beta = \frac{ch}{oc} \Rightarrow ch = oc \cos\beta$$

$$Cd + dh = I_p \cos\beta$$

$$\frac{I_s}{n} \cos\alpha + I_c = I_p \cos\beta \longrightarrow ③$$

$$\sin \beta = \frac{oh}{oc} \Rightarrow oh = oc \sin \beta$$

$$o_i t_i h = I_P \sin \beta$$

$$I_m + \frac{I_s}{n} \sin \Delta = I_p \sin \beta \longrightarrow (4)$$

→ consider large triangle Lab,

$$\cos \theta = \frac{oa}{ab} \Rightarrow oa = ob \cos \theta$$

$$V_p \cos\theta = \frac{OA}{\cos\theta + g^2} \quad [\text{writing into striking, multiply with } \cos\theta \text{ & sin}]$$

$\therefore OA$ becomes from the

$$V_p \cos\theta = nV_s + nI_s r_s \cos\Delta + nI_s x_s \sin\Delta + I_p x_p \cos\beta + I_p x_p \sin\beta$$

(S)

$$nV \cos \theta = 1$$

$$V_p = nV_s + nI_s x_s \cos \Delta + nI_s x_s \sin \Delta + I_p x_p \cos \beta + I_p x_p \sin \beta$$

"B" in terms of "A"

$$V_p = nV_s + nI_s x_s \cos \Delta + nI_s x_s \sin \Delta + \left[\frac{I_s}{n} \cos \Delta + I_c \right] x_p + \left[I_m + \frac{I_s}{n} \sin \Delta \right] x_p$$

[∴ from (3) & (4)]

$$V_p = nV_s + I_s \cos \Delta \left[n x_s + \frac{x_p}{n} \right] + I_s \sin \Delta \left[n x_s + \frac{x_p}{n} \right] + x_p I_c + x_p I_m$$

by taking "n" as 1cm; $n^2 x_s + x_p = R_o$
∴ $n^2 x_s + x_p = x_o$

$$V_p = nV_s + \frac{I_s}{n} R_o \cos \Delta + \frac{I_s}{n} x_o \sin \Delta + x_p I_c + x_p I_m$$

$$V_p = nV_s + \frac{I_s}{n} \left[R_o \cos \Delta + x_o \sin \Delta \right] + I_c x_p + I_m x_p$$

∴ Actual Ratio $R = \frac{V_p}{V_s}$

$$R = n + \frac{\frac{I_s}{n} \left[R_o \cos \Delta + x_o \sin \Delta \right] + I_c x_p + I_m x_p}{V_s}$$

referred to primary

→ Actual Ratio referred to secondary

$$R = n + nI_s \left[R_o \cos \Delta + x_o \sin \Delta \right] + I_c x_p + I_m x_p$$

referred to secondary

for phase angle, (θ)

$$\text{consider } \angle \text{ab} ; \tan \theta = \frac{ab}{oa}$$

$$\tan \theta \approx 0$$

$$\theta = \frac{I_p X_p \cos \beta - I_p \gamma_p \sin \beta + n I_s \gamma_s \cos \Delta - n I_s \gamma_s \sin \Delta}{n V_s + n I_s \gamma_s \cos \Delta + n I_s \gamma_s \sin \Delta + I_p \gamma_p \cos \beta + I_p \gamma_p \sin \beta}$$

neglected

$$\theta = \frac{I_p X_p \cos \beta - I_p \gamma_p \sin \beta + n I_s \gamma_s \cos \Delta - n I_s \gamma_s \sin \Delta}{n V_s + \left[\frac{\pi}{2} + \tan^{-1} \left(\frac{n V_s}{I_p \gamma_p} \right) \right] + \tan^{-1} \left(\frac{n I_s \gamma_s}{I_p \gamma_p} \right)}$$

" β " instead of " Δ " in $\tan^{-1} \left(\frac{n V_s}{I_p \gamma_p} \right)$ present yet

$$\theta = \frac{X_p \left[\frac{I_s}{n} \cos \Delta + I_c \right] - \gamma_p \left[\frac{I_s}{n} \sin \Delta + I_m \right] + n I_s \gamma_s \cos \Delta - n I_s \gamma_s \sin \Delta}{n V_s}$$

$$\theta = \frac{I_s \cos \Delta \left[\frac{X_p}{n} + n \gamma_s \right] - I_s \sin \Delta \left[\frac{\gamma_p}{n} + n \gamma_s \right] + I_c X_p - \gamma_p I_m}{n V_s}$$

at $\tan^{-1} \left(\frac{n V_s}{I_p \gamma_p} \right) + \left[\frac{\pi}{2} + \tan^{-1} \left(\frac{n I_s \gamma_s}{I_p \gamma_p} \right) \right]$

$$\theta = \frac{\frac{I_s}{n} X_{01} \cos \Delta - \frac{I_s}{n} R_{01} \sin \Delta + I_c X_p - \gamma_p I_m}{n V_s}$$

$$= \frac{I_s}{n} \left[X_{01} \cos \Delta - R_{01} \sin \Delta \right] + I_c X_p - \gamma_p I_m$$

phase of inductive voltage formula

$$\therefore \theta = \frac{180}{\pi} \left[\frac{I_s}{n} \left[X_{01} \cos \Delta - R_{01} \sin \Delta \right] + I_c X_p - \gamma_p I_m \right] \text{ degrees}$$

There are two types of errors

① Ratio error

② Phase angle error.

$$\% \text{ Ratio error} = \frac{K_n - R}{R} \times 100$$

$$\text{where, } R = n + \frac{I_s}{n} [R_o \cos \Delta + X_o \sin \Delta] + I_c X_p + I_m X_p$$

$$\text{Phase angle error}(\theta) = \frac{180}{\pi} \left[\frac{\frac{I_s}{n} [X_o \cos \Delta - R_o \sin \Delta] + I_c X_p - I_m X_p}{n V_s} \right]$$

$$X_o = 3$$

$$R_o = 10 \Omega$$

$$A\Delta = m^\circ ; A\theta = p^\circ$$

11/12/19 $n = \frac{N_2}{N_1} = \frac{I_1}{I_2}$ ~~899~~

A current TLF has turns ratio 1:399 and is rated as 2000/5A. The core loss component is 3A & magnetising component is 8A under full load conditions. Find phase angle and ratio errors if secondary circuit power factor is 0.8 leading.

Sol: Given data,

$$n = \frac{N_s}{N_p} = \frac{I_p}{I_s}$$

$$n = \frac{N_s}{N_p} = \frac{399}{1} \quad \left. \begin{array}{l} \text{primary high curr} \\ \text{secondary low curr} \end{array} \right\}$$

$$\rightarrow K_n = \frac{I_p}{I_s} = \frac{2000}{5} = 400$$

$$I_c = 3A ; I_m = 8A$$

Find: $\theta = ?$

$$\rightarrow \% \text{ ratio error} = \frac{K_n - R}{R} \times 100$$

$$\rightarrow \cos \delta = 0.8 \text{ lead}$$

$$\delta = -36.86$$

$$\theta = \frac{180}{\pi} \left[\frac{I_m \cos \delta - I_c \sin \delta}{n I_s} \right]$$

$$I_c = 3A$$

$$I_m = 8A$$

$$\rightarrow \text{Actual Ratio } (R) = n + \frac{I_m \sin \delta + I_c \cos \delta}{I_s}$$

$$= 399 + \frac{(8)(-0.6) + (3)(0.8)}{5}$$

$R = 398.52$

$$\cos \delta + I_m \sin \delta$$

$$\% \text{ Ratio error} = \frac{k_n - R}{R} \times 100$$

$$= \frac{400 - 398.52}{398.52} \times 100$$

$$= 0.371\%$$

$$\rightarrow \text{phase angle } (\theta) = \frac{180}{\pi} \left[\frac{I_m \cos \delta - I_c \sin \delta}{n I_s} \right]$$

$$= \frac{180}{\pi} \left[\frac{8(0.8) - (3)(-0.6)}{399 \times 5} \right]$$

$$= 0.235^\circ \approx 13.46'$$

A current T/F with 5 primary turns has a secondary burden load consisting of a resistance of 0.16Ω & inductive reactance of 0.12Ω .

when the primary current is $200A$, the magnetising current is $1.5A$, the core loss current is $0.4A$. Find the no. of turns on secondary needed to make the current ratio $100:1$

and phase angle.

Sol: Given data,

$$N_p = 5 \text{ turns}$$

$$R_e = 0.16 \Omega ; X_e = 0.12 \Omega$$

$$I_p = 200A$$

$$I_m = 1.5A ; I_c = 0.4A$$

$$\text{Find:- } N_s = ?$$

$$\Rightarrow \delta = \tan^{-1} \left(\frac{X_e}{R_e} \right) = \tan^{-1} \left(\frac{0.12}{0.16} \right) = 36.86^\circ$$

$$1.0 = 200 : 5 : 1$$

$$\Rightarrow \frac{I_p}{I_s} = 100.1$$

$$I_s = 1.998 A$$

$$\Rightarrow \frac{N_s}{N_p} = n \Rightarrow 100.1$$

$$N_s = N_p \times 100.1$$

$$N_s = 500.5 \text{ turns}$$

$$\theta = \frac{180}{\pi} \left[\frac{I_m \cos \delta - I_c \sin \delta}{n I_s} \right]^\circ$$

$$\theta = \frac{180}{\pi} \left[\frac{1.5 \times 0.8 - 0.4 \times 0.6}{100.1 + 1.998} \right]^\circ$$

$$\theta = 0.275^\circ$$

A current T/F of turns ratio of 1:199 is rated as 1000/5A, 1.25VA. The core loss is 0.1W & magnetising current is 7.2A. Determine phase angle & ratio errors for rated load & rated secondary current at 0.8 power factor lagging.

(ii) at 0.8 " " leading.

$$n = \frac{N_s}{N_p} = \frac{199}{1}$$

Sol: Given Data:-

$$n = \frac{N_s}{N_p} = \frac{199}{1} = 199$$

$$\rightarrow 1000/5A \Rightarrow K_n = \frac{I_p}{I_s} = \frac{1000}{5} = 200$$

\rightarrow power rating = 25VA

\rightarrow core loss = 0.1W

$$I_m = 7.2A$$

In T/F, power is same. But voltage & current \uparrow (2) times

Find :-

$$\theta = ?$$

$$\therefore R = \frac{K_n - R}{R}$$

Process to find :-

In Transformer, power is same i.e.,

$$E_p I_p = E_s I_s = 25 \text{ VA}$$

$$\therefore E_p I_p = 25 \text{ VA} \quad | \quad E_s I_s = 25 \text{ VA}$$

$$\text{Given } E_p = \frac{25}{1000} = 0.025 \quad | \quad E_s = \frac{25}{5} = 5 \text{ V}$$

To know the core component current (I_c), core loss power is 0.1 W . core loss present at primary, so take relation as

$$\text{Core loss power} = E_p I_c$$

$$\therefore I_c = \frac{0.1}{0.025} = 4 \text{ A}$$

$$\therefore I_c = 4 \text{ A}$$

(i) Actual Ratio

$$R = n + \frac{I_m \sin \delta + I_c \cos \delta}{I_s}$$

$$= 199 + \left(\frac{7.2 \times 0.6 + 4 \times 0.8}{5} \right)$$

$$R = 200.504$$

[condition 0.8 lagging (+)]

$$\cos \delta = 0.8$$

$$\delta = 36.86$$

$$\sin(36.86) = 0.6$$

$$\therefore \text{Ratio error} = \frac{K_n - R}{R} \times 100$$

$$= \frac{200 - 200.504}{200.504} \times 100$$

$$= -0.251 \%$$

$$\rightarrow \theta = \frac{180}{\pi} \left[\frac{I_m \cos \delta - I_c \sin \delta}{n I_s} \right]$$

$$= \frac{180}{\pi} \left[\frac{7.2 \times 0.8 - 4 \times 0.6}{199 \times 5} \right]$$

$$\theta = 0.193^\circ$$

(ii) 0.8 leading (-)

$$R = n + \left[\frac{I_m \sin \delta + I_c \cos \delta}{I_s} \right] \quad \text{cos}(88) = 0.8 \quad \delta = -36.86$$

$$= 199 + \left\{ \frac{7.2(-0.6) + 4 \times 0.8}{5} \right\}$$

$$R = 198 - 78$$

• Ratio error = 0.615%.

$$\text{Phase Angle}(\theta) = 0.469^\circ$$

$$h\mu = \sum_{i=1}^n \lambda_i$$

~~Logging (true)~~

~~cos s = d/cos s = sin s / (-v)~~

Q2 At its rated load of 25VA, (100/5) current transformer has.

Iron loss of 0.2 W, and magnetising current is 1.5 A, calculate its ratio error & phase angle when supplying rated output to a meter having a ratio of resistance to reactance of 5.

Given Data:-

$$\text{power rating} = 25 \text{ VA}$$

$$K_n = \frac{100}{5} \text{ A} = \frac{I_p}{I_s}$$

$$\text{iron loss} = 0.2 \text{ W}$$

$$I_m = 1.5 \text{ A}$$

$$n = \frac{I_p}{I_s} = \frac{100}{5} = 20$$

$$\frac{I_p}{I_s} = \frac{N_s}{N_p}$$

$$\rightarrow \text{on T/F; } E_p I_p = E_s I_s = 25 \text{ VA}$$

$$\begin{aligned} E_p I_p &= 25 \\ E_p &= \frac{25}{100} \\ &= 0.25 \end{aligned} \quad \left| \begin{array}{l} E_s I_s = 25 \\ E_s = \frac{25}{5} \\ E_s = 5 \end{array} \right.$$

$$\begin{aligned} &\text{on T/F; } E_p I_p = E_s I_s = 25 \text{ VA} \\ &E_p I_p = 25 \text{ VA} \\ &I_c = 0.2 \text{ W} \\ &I_m = 1.5 \text{ A} \end{aligned}$$

$$\rightarrow \text{iron loss power} = E_p I_c$$

$$I_c = \frac{0.2}{0.25} = \left[\frac{251.0 \times 3.0 - 8P.0 \times 2.1}{2+0.5} \right] 0.81 =$$

$$I_c = 0.8 \text{ A}$$

$$0.825 \cdot 0 = 0$$

$$\rightarrow \frac{R_e}{X_e} = 5$$

$$S = \tan^{-1} \left(\frac{X_e}{R_e} \right) = \tan^{-1} \left(\frac{1}{5} \right)$$

$$S = 11.309^\circ$$

$$\cos f = \cos(11^\circ 30') = 0.98$$

$$\sin \delta = \sin(11.309) = 0.196$$

$$\therefore f = n + \text{Im} \sin \delta + \text{Im} \cos \delta$$

15

$$= 90 + 1.5 \times 0.196 + 0.8 \times 0.98$$

5

$$R = 20.9156$$

$$\text{Ratio error} = \frac{K_n - R}{R} \times 100$$

R.

$$= \frac{20 - 20.2156}{20.2156}$$

$$\text{Ratio}_{\text{good}} = -1.066 \cdot 1.$$

$$\theta = \frac{180}{\pi} \left[\frac{I_m \cos \delta - I_c \sin \delta}{n I_c} \right]$$

$$= \frac{180}{\pi} \left[\frac{1.5 \times 0.98 - 0.8 \times 0.196}{20 \times 5} \right]$$

$$\theta = 0.752^\circ$$

$$4.8 \cdot 0 = 0$$